

NOVEMBER
1955

A TRANSMITTER WITH LOW HARMONIC OUTPUT
V.H.F. AUTOMATIC TUNER . . . LIGHTNING PROTECTION FOR
THE ANTENNA . . . ANTI TVI FILTERS . . . V.H.F. CONTEST RULES

Amateur Radio

AMATEURS AND TECHNICIANS!

This is the BEST SPOT in Melbourne for . . .

RADIO PARTS AND ACCESSORIES!

Distributors of ADVANCE, PALEC, TAYLOR, and
UNIVERSITY Meters and Test Equipment.

And such well-known Radio
Accessories as . . .

- AEGIS products
- TRIMAX products
- A & R products
- FERGUSON products
- ROLA products
- JENSON products
- I.R.C. products
- ALPHA products
- CYLON products
- B.S.R. products
- MORGANITE Potentiometers
- STENTORIAN Speakers
- STEANE'S Amplifiers
- SUPERSPEED SOLDER
- GOLDRING products
- CONNOISSEUR products
- EDDYSTONE products
- M.S.P. products
- BELLING-LEE products
- DUCON products
- SIMPLEX products
- BULGIN products
- OAK products
- LEAK Amplifiers
- QUAD Amplifiers
- RADIOTRON Valves
- PHILIPS Valves
- BRIMAR Valves
- MONARCH Gramo. Motors
- GARRARD Gramo. Motors
- COLLARO Motors, Pickups



1/-



208 LT. LONSDALE ST., MELB.

PHONE: FB 3731 — OPEN SATURDAY MORNINGS!

"HAM" RADIO SUPPLIERS

(KEN MILBOURN, PROP.)

BARGAINS GALORE. COMPARE THESE PRICES

PROMPT ATTENTION TO YOUR NEEDS.

NEVER CLOSED BETWEEN 9 A.M. AND 5.30 P.M.

Command Transmitters: Freq.: 4-5.3 Mc., 5.3-7 Mc., or 7-9 Mc.
Complete with valves and crystal £7/10/-

AT5 Transmitters, covers low freq. bands, also bandswitched
3 bands 2-20 Mc. using 6V6 M.O./xtal osc., 807 buffer/dbler.,
pair 807s in parallel; 6V6 grid mod. All stages metered with
0-5 Ma. meter (250 Ma. F.S.D.); a gift at £3

AT5-AR8 Junction Box and Cables £2/10/-

AR8 Cables 7/6 each

AT5-AR8 Aerial Coupling Units, contain one 0-5 Ma. meter
ext. thermo couple, single gang variable condenser, keying
relay, aerial change-over d.p.d.t. 12v. 48 ohm relay, etc. Ideal
for wrecking. A Bargain at £1/10/-

English Rebecca Transceivers, new, turret tuned. Contains 17
valves: EF50, 884, 6SN7, VR150, RL37, RL18, VR135, 2050,
5V4. Plug-in 28 Mc. EF50 I.F. strip. Plug-in turrets. Six
bands, approx. 200 Mc. Unit complete and packed in case
ready for rail. No packing charge £9/10/-

WANTED TO BUY: RECEIVERS, TRANSMITTERS, VALVES, ETC.

English 5BP1 CRO Indicator, new, complete with seven EF50
valves, one 879, one VR54, and one 6H6. Packed in case
ready for rail. No packing charge £8/10/-

U.S.A. I.F.F. Units, comp. with valves, less genemotor, £4/17/6

Meters—0-100 microamp. heavily damped, 2½ inch round.
Calibrated 0-1500 linear scale £2

Meters—0-20v., 5 Ma. movement, square type, 2 inch, new, 15/-

Meters—0-2.5 Amp. R.F., square type, 2 inch, new 15/-

Meters—0-5 Ma., 1½ Ma. movement, round 2" type, new, 22/6

Phone Plug and Cable (4 ft.) American 4/6

Phone Plug and Cable (6 ft.) Australian 3/6

Output Transformers, well known make, 6,000 ohms c.t. to
600 ohms, 40 Ma. Max. level 30 db., new, to clear 35/-

Command Receivers, 6-9 Mc. range, less genemotor; air
tested £7/10/-

Command Receiver Racks, twin, brand new in cartons, includes
two relays, switches, phone sockets, etc. £1

Command Receiver Right-angle Drives 2/6

Command Receiver Flexible Drives, 12 ft. long 11/-

AR8 Receivers, 11 valves, 6 bands, continuous coverage 150
Kc.-25 Mc., BFO, audio controls, calibrated dials £15

AR301 High Freq. Receiver, uses three 954s, one 955, six 6AC7
I.F. stages at 30 Mc. Converts to 144 Mc. Complete, £6/10/-

Canadian type AR301 V.h.f. Receiver, uses 3-954, 1-955, six
6AC7 I.F. stages at 30 Mc. Easily converted to 144 Mc.
New, in case £8/10/- F.O.R.

BC733D Crystal Locked Receiver. Tuning range 108-120 Mc.
I.F. 6.9 Mc. Valve line-up: three 717As, two 12SG7s, one
12SH7, two 12SR7s, one 12SQ7, one 12A6. Also contains six
miniature relays, less xtal. Packed ready for rail. £5 each.

American Low Freq. and Broadcast Band Receiver, RAX, 7
valves, 4 bands: 200-300 Kc., 300-500 Kc., 500-900 Kc., 900-
1500 Kc. I.F. 160 Kc. Calibrated vernier dial, etc. Ideal
Q5'er. Complete with 28v. genemotor £17/10/-

LARGE RANGE OF VALVES AND CRYSTALS IN STOCK

Aust. Wavemeter Type AWB1, high freq. 145 to 165 Mc. approx.
Valve line-up: 958 diode connected into two type 1N5 valves
cascode connected d.e. amp. Complete with spare set of valves
and 3 inch 0-1 Ma. meter. Circuit enclosed. Contained in flat
grey metal carrying case. Packed ready for rail, £5/17/6

Six volt bayonet type Dial Lamps 1/- each

American Headphones, low imped., complete with cable, 25/-

American Loran Indicators. Contains 26 valves including 14-
6SN7, 2-6SL7G, 9-6H6, 1-6SJ7 and 5CP1 C.R.O. tube. Com-
plete with 100 Kc. R.C.A. Xtal and Valves £15

5FP7 5 inch electromagnetic deflection with socket housing,
deflecting coils and controls £3

5A MELVILLE STREET, HAWTHORN, VICTORIA

North Balwyn Tram Passes Corner, near Vogue Theatre.

Phone: WA 6465

Money Orders and Postal Notes payable North Hawthorn P.O. Packing Charge on all goods over 10 lbs. in weight, 5/- extra.

AMATEUR RADIO

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA

EDITOR:

T. D. HOGAN, VK3HX.

MANAGING EDITOR:

J. G. MARSLAND, VK3NY.

TECHNICAL EDITOR:

K. E. PINCOTT, VK3AFJ.

TECHNICAL STAFF:

J. C. DUNCAN, VK3VZ.

D. A. NORMAN, VK3UC.

R. S. FISHER, VK3OM.

COMPILATION:

R. W. HIGGINBOTHAM, VK3RN.

CIRCULATION:

I. K. SEWELL, VK3IK.

ADVERTISING REPRESENTATIVE:BEATRICE TOUZEAU,
98 Collins St., Melbourne, C.I.
Telephone: MF 4505**PRINTERS:**"RICHMOND CHRONICLE."
Shakespeare St., Richmond, E.I.
Telephone: JB 2419.

MSS. and Magazine Correspondence should be forwarded to the Editor, "Amateur Radio," C.O.R. House, 191 Queen Street, Melbourne, C.I., on or before the 8th of each month.

Subscription rate in Australia is 12/- per annum, in advance (post paid) and A15/- in all other countries.

Wireless Institute of Australia
(Victorian Division) Rooms' Phone
Number is MY 1087.

WI BROADCASTS

All Amateurs are urged to keep these frequencies clear during, and for a period of 15 minutes after, the official Broadcasts.

VK3WI: Sundays, 1100 hours EST, 7146 Kc. and 2000 hours EST 59 and 144 Mc. No frequency checks available from VK3WI. Intra-state working frequency, 7125 Kc.

VK3WI: Sundays, 1120 hours EST, simultaneously on 3573 and 7146 Kc., 51,016 and 144.25 Mc. Intra-state working frequency 7125 Kc. Individual frequency checks of Amateur Stations given when VK3WI is on the air.

VK4WI: Sundays, 0900 hours EST, simultaneously on 3550 and 1434 Kc. 5000 Kc. channel is used from 0915 hours to 1015 hours each Sunday for the W.I.A. Country hook-up. No frequency checks available.

VK5WI: Sundays, 1000 hours EAST, on 7146 Kc. Frequency checks are given by VK5MD and VK5WI by arrangements on all bands to 50 Mc.

VK6WI: Sundays, 0930 hours WEST, on 7146 Kc. No frequency checks available.

VK7WI: Sundays, at 1000 hours EST, on 7146 Kc. and 144.5 Mc. No frequency checks are available.

VK8WI: Sundays, 1000 hours EST, simultaneously on 3.5, 7, 14 and 144 Mc. Individual frequency checks of Amateur Stations given when VK8WI is on the air.

Published by the Wireless Institute of Australia,
C.O.R. House, 191 Queen Street,
Melbourne, C.I.

GUEST EDITORIAL



"Nation Shall Speak Peace Unto Nation"

runs the inscription over the portals of the B.B.C. Headquarters in London.

It was with mixed feelings that one listened to sundry broadcasts on the "Big Four" "pow-pow" at Geneva. At that slightly sinister gathering of individuals in whose hands the very existence of civilisation balanced precariously, the result was hailed by newscasters far and wide, to the effect that the "future outlook for negotiations is less brittle!"

Memory surges back to Munich, with hopes of "peace in our time," and the ranting fulminations from Zeesen by one in whose hands the peace then lay. It is difficult to believe that today, those on one side of the fence are contemplating the other in benignity for h.f. radio channels indicate otherwise.

The state of affairs in most of our 40 metre allocation is ironical. In view of the aura of goodwill displayed at Geneva, perhaps one may be pardoned for wondering why those saw-tooth oscillators driving megawatts of pulsed power have been, and still are, weaving their belligerent pattern?

For years now the "cold war" has included this radio version, with the skipping about of "QRM factories,"

whilst the B.B.C., and others, try to dodge by frequency "cuddling." This goes on in the a.w.l. 31, 25 and 19 metre bands, but probably with severest intensity in our 150 Kc. of "40." From 7100 Kc. higher, is torn to shreds by juggernauts with no heed for Amateur Radio.

If leaders of nations in this world are sincere about goodwill, effective procedure would be to ensure unhindered inter-communication between youth of all nations. It should be a top priority.

The present restricted frequency snippets in the useful DX regions should be superseded by far more generous allocations. Amateur Radio should be given scope to spread its beneficial influence throughout the younger generations, with bands wide enough to permit congestion-free DX working. Is it too much to hope that there may yet arise statesmen with enough foresight and courage to realise that non-commercial communication between individuals by the medium of Amateur Radio can be a potent factor for future international understanding and the effective removal of man-made barriers?

—D. B. KNOCK, VK3 Division.

THE CONTENTS

A Transmitter with Low Harmonic Output, Part II	2	Ross Hull Memorial V.h.f. Contest, 1955-56	14
A V.h.f. Automatic Tuner	5	Olympic Games Communication Demonstration	15
Lightning Protection for the Transmitting Antenna	7	VK3 Award for 100 V.h.f. Contacts	17
Prediction Chart for Nov., 1955	8	Fifty Megacycles and Above	15
Use of Electronic Valves	9	DX Activity by VK3AHH	19
Anti TVI Filters for the Amateur Transmitter	10	Federal, QSL, and Divisional Notes	20
		Correspondence	24

A Transmitter With Low Harmonic Output

PART TWO

BY HANS RUCKERT,* VK2AOU

POWER AMPLIFIER STAGE

Fig. 3: The plate circuit of the driver valve and the grid circuit of the p.a. are equipped with multiband tank circuits which are ideal for this purpose. No bulky coil switching is required. A simple small split-stator variable capacitor of 2×100 pF. and two fixed coils are all that is needed to cover the range from 3.2 to 34 Mc.

When adjusting the coils of these tanks it is important to make sure that the 3.5 and 14 Mc. and the 7 and 28 Mc. settings of the variable capacitor are not the same. If they are, the stage may not only amplify the lower frequency, but may also act as a frequency multiplier, upsetting the purpose of the stage. This test can be easily carried out with a grid dip meter.

Two link lines with coax cable are needed, one for the small coils and one for the two big coils. The highest voltage is always at the spot where the two coils meet (hot end), but the inductive coupling has to be done with two links. The 3.5 and 7 Mc. band uses the big coil (30 turns), whilst 14, 21 and 28 Mc. use the small coil (13 turns).

These two multiband tanks can be coupled with the link lines so closely that again a band-filter effect is achieved, permitting a change of oscillator frequency over a certain range without having to retune the driver multiband tanks.

The two Telefunken valves LS50 are all-glass radar pulse valves with about the same ratings as the 807, but they have half the volume. With 100 watts input the valves are not fully loaded, but this is a precaution against overload and damage to the cathodes if by accident the tank should be too properly tuned or the coupling should be too tight.

The regulated grid bias is set to -130v. The screen voltage can be reduced from 250v., normally, to 150v. for tuning purposes. To achieve effective and low distortion modulation, it is necessary to modulate the screen grid as well. This can be easily carried out by putting a small power supply choke (20 hr. at 30 Ma.) in the screen grid lead and by-passing the screen grids only for r.f. with a 1000 pF. capacitor each.

To prevent any self oscillation of the p.a. stage, if the antenna is switched off when receiving, the "T or R" relay disconnects the screen supply. No neutralisation was required.

The best parallel feeding choke is still by far the single layer coil of about $\frac{1}{2}$ " diam. and about 60 turns to get 180 uH. This choke represents about 100,000 ohms impedance over the range from 3 to 35 Mc. without showing any resonances in this range. Usually r.f. chokes have far too much inductance and sharp pronounced series and parallel resonance. It is hopeless to use those chokes with different coils in series

because you never know if you have 3,000,000 or 3,000 ohms impedance on the different bands. Multilayer coil chokes are very likely to go up in smoke.


Three ceramic high voltage disc capacitors of 250 and 500 pF. are used to couple the pi-tank to the p.a. or to by-pass r.f. behind the two r.f. chokes. These t.v.-type capacitors are very small and their breakdown voltage is near 30kv. d.c.

The pi-filter is also band-switching. This version of the old Collins filter with its 70 ohm impedance parallel to the output capacitor has several important features: Band-switching is easily done because no coupling coils have to be changed. The 28 Mc. coil is used in place of the lead from the main tuning capacitor to the switch around which the two other coils are arranged. $\frac{1}{2}$ " wide silvered copper strips are used

The place for the low-pass filter is only marked on this circuit. The filter has a cut-off frequency of 35 Mc. and high attenuation from 41 Mc. and higher of at least 50 db. to suppress the third harmonic of 14 Mc., the second harmonic of 21 Mc. and also other harmonics which may otherwise get out to the aerial. No measurable losses by inserting the filter have been found and only the coils of the filter did show a very slight increase in temperature whilst the NPO ceramic disc type capacitors remained cold (power factor better than 0.04% on short waves). This filter will be described in all details in a later article.

ANTENNA COUPLER

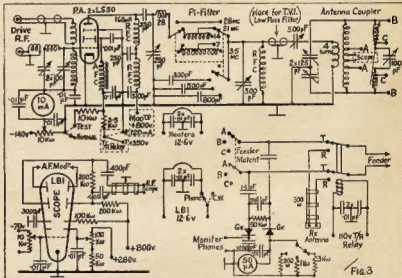To feed any feedline from this transmitter with an unsymmetrical p.a. and pi-filter tank, to assist the low-pass filter in suppressing harmonics, and to



Erratum.—The p.a. stage should show two tubes in parallel. The circuit components are designed to operate under these conditions. Each p.a. tube screen is separately by-passed.

as leads to reduce inductance to wire the pi-network. A ganged three wafer switch with heavy spring contacts (five per wafer on the same contact) changes the coils or taps on the coils and connects also different fixed ceramic capacitors parallel to the output variable capacitor. This capacitor is a 500 pF. receiver type because at 70 ohms we are not likely to have a higher r.f. voltage than 100 volts parallel to this capacitor, even with some mismatch.

Maximum output from the pi-network is obtained with about 300 pF. output capacity at 28 Mc., 400 pF. at 21 Mc., 550 pF. at 14 Mc., 800 pF. at 7 Mc., and 1,200 pF. at 3.5 Mc. A mismatch in the antenna coupler or feeder of the aerial is certain if very much smaller capacity values are giving better results.

have a simple means to couple r.f. to the scope for modulation control, an antenna coupler was used. Here again a multiband tank circuit was employed so that no coil changing or switching of turns was required.

The writer did not have the often-used four-gang capacitor for tuning this symmetrical multiband tank, so the split-stator capacitor between the halves of the small coil was replaced by a single air capacitor using a ceramic extended spindle. For 3.5 to 7 Mc. the hot ends of this tank are the ends of the big coil at "B," here we would have to connect tuned feeders, but 300 or even 70 ohm feeders would be connected closer to the centre of the big coil at "A." The centre of this coil is always r.f. cold, and here we couple the four-turn link, coming from the

*25 Berrille Road, Beverly Hills, N.S.W.

p.a. stage or low-pass filter, via the 500 pF. variable capacitor to the antenna coupler.

This single fixed link is a satisfactory compromise for all bands from 3.5 to 28 Mc. and helps to simplify the matter a great deal. The feeders for the higher frequency bands, like 14 to 28 Mc., have to be put on the two small coils symmetrically. Only the 28 Mc. feeder may be in some cases also placed on the big coil.

The small coils are nearly r.f. cold at their outside ends, but hot at the 100 pF. capacitor "C." The two halves are closely coupled to each other. They are like a single coil with an interruption in the middle. They have to handle all the power at 14 to 28 Mc. and should be wound with heavy wire or tubing.

If the coils of the coupler get hot, then not much power is being transferred to the aerial but is being lost due to mismatch and standing waves. Try different taps.

The writer was using a 130 ft. Zepp antenna for all bands with this coupler and a piece of double co-ax cable 22 ft. long. This cable acted as a quarter wave tuned feeder on 7 Mc., and tuning with the coupler, it worked similarly at 3.5 Mc. or any other band up to 30 Mc. The same coupler and piece of double co-ax cable was used as a part of the 70 ohm feeder, extended by 70 ohm twin lead cable, to operate a three element 14 Mc. beam. The shielding of the cable was earthed and helped to prevent the radiation of r.f. from the feeder to other cables and gear in the shack, an important part of the efforts to reduce b.c.l. and t.v.i.

CHECKING MODULATION

It is extremely simple to install a scope to check the modulation. The author would not like to operate a phone transmitter without a scope, because before we can hear distortion and splatter, we may be most likely causing trouble to fellow Amateurs.

The scope uses the same power source as the p.a. stage. In this case the deflection plates have to be put on high tension, too. The r.f. deflection plates of the scope (Telefunken type LBI 23 diameter screen) are coupled to two high voltage ceramic disc type capacitors of 400 pF. and a piece of double co-ax cable to the antenna coupler.

In the receiving position the scope gets a high negative bias so that the screen cannot get burnt.

A section of Fig. 3 shows the circuit of the scope and in another section the output connections with the antenna relay, etc., can be seen. The switch positions A, B or C indicate the different connections the antenna relay can have to the antenna coupler coils, depending on the type of feeder or aerial used. The same aerial is used for the receiver which is connected to the relay via 300 ohm double co-ax cable.

After the thermocouple meters had been burnt out when making tests much earlier, the writer decided to use Ge diodes to measure the r.f. voltage instead of the current. Now two 1.5 pF. bead type ceramic capacitors take a small amount of r.f. to the diodes where one acts as rectifier to feed a headphone to monitor the phone transmission, and the other diode forms the r.f. voltmeter

together with a 50 microamp. instrument. This method is just as good and most likely more accurate at 30 Mc. because not many thermocouple amp-meters are correct over a frequency range of more than 1:3.

GENERAL REMARKS

Before concluding the description of the h.f. part of the transmitter, a few more general remarks may be made. The v.f.o., the five frequency multiplier stages, and the driver stage are built on one chassis, using three sub-chassis, which are arranged in such a way that the v.f.o. and driver are close to the front panel and the multipliers are at the back of the chassis. In the middle are the a.f. stages of the modulator pre-amplifier and the stages of the clipper filter.

The upper chassis carries the p.a. and the antenna coupler, whilst the scope is in the middle and the modulator final is built at the back of the chassis. There are several shielding compartments.

In both chassis all wiring, except certain h.f. leads, is done with shielded wire or co-ax cable. This takes much more time to do, but it pays in the time saved looking for r.f. or a.f. where they should never be. This very important step, together with effective by-passing, using entirely ceramic disc type capacitors, is so necessary to confine r.f. generally, and harmonics especially, to the chassis compartments where they have been generated.

That is why even a very sensitive absorption type frequency meter with a Ge diode and 100 microamp. meter will not detect any harmonics at the grid of the driver, the grid circuit is not tuned to. The same applies to the driver plate and p.a. plate circuit.

All capacitors up to 0.05 uF. are ceramic dielectric capacitors. It may have been even better to use 1,000 pF. and not 10,000 pF. by-pass capacitors to work closer to the self-resonance frequency of these by-pass capacitors. These are so small that 30 would not require more space than a cigarette.

It would be of little value to give accurate coil winding data because a different layout, other capacitors or valves would cause too great variations. The multiplier stages use receiver type plastic coil formers where a plastic screw holds a short wave iron slug. These formers are 1/2" diameter. The coupling of the band-filter coils has to be made as tight as possible, especially at 3.5 and 7 Mc. as it would have been impossible to achieve enough coupling without the slugs. This would be simpler if a bigger coil diameter is used. These coils have no stray field because they are so small and the slug helps, too, in this regard.

The coils of the three multiband tank circuits and those of the pi-network are at first wound as estimated, using some old wire of a burnt out transformer. Checking with the grid dip meter shows if the turns are right or if the diameter and coil length have to be changed. When the proper coil dimensions are found, which does not take long with a calibrated grid dip meter, the right wire gauge or copper tubing may be used. In this way all stages can be aligned without switching the transmitter on.

"WILLIS" CHASSIS PUNCHES



Manufactured especially for the Radio and Electrical Engineer and Constructor. Gives that clean cut professional appearance.

3/8"	21/-	1-1/8"	33/6
1/2"	22/6	1-3/16"	35/-
5/8"	22/6	1-1/4"	47/6
11/16"	23/6	1-1/2"	47/6
3/4"	24/6	2"	62/6
1"	31/6		

Special Sizes Made to Order.

Made of Finest Quality Tool Steel.
Guaranteed 10,000 Holes.



BRITISH "Q-MAX" SCREW TYPE CHASSIS CUTTERS

5/8"	24/3	1-3/4"	38/4
3/4"	24/3	2-3/32"	62/6
7/8"	26/8	1-1/4"	42/6
1"	31/8	1" Square	47/11
1-1/8"	31/8		
1-1/4"	31/8	Spare Keys	
1-3/8"	35/-	All Sizes	1/6
1-1/2"	35/-		

The Ideal Chassis Hole Cutter
where equipment is already
mounted.



The Famous "WILLIAMSON" AMPLIFIER OUTPUT TRANSFORMERS

British "Woden" Manufacture
to exact specifications
as advertised on front pages of
"Williamson" Amplifier Handbook

"WODEN"

A High Quality Name in British
Transformer Design
AVAILABLE FROM STOCK NOW
Price retail £19/18/6

Trade Enquiries Invited



WILLIAM WILLIS
& CO. PTY. LTD.

428 BOURKE ST., MELB'NE

Phone: MU 2426

ZEPHYR MICROPHONES



"THE MICROPHONE THAT SPEAKS FOR ITSELF"

TYPE "30"

A high quality Moving Coil Microphone of striking appearance and fidelity.

- Ideal for transmission of voice or music.
- Good appearance.
- Solid cast case, finished in stoved black enamel, full tilting head.



TYPE "30"
MOVING
COIL

TYPE "8XA"

A quality Crystal Insert with "Zephyrifil" filter.

- Durable chrome steel cage.
- Hand or stand pattern.
- Good high frequency response.
- Full tilting head.



TYPE "8XA"
CRYSTAL



TYPE "40"
RIBBON



TYPE "90"
MOVING
COIL

TYPE "40"

A high grade Studio Microphone, reasonably priced, for those requiring high fidelity.

- Imported magnets, highly efficient generator.
- Fully protected against dust and filings.
- Rotatable cage—360°.
- Chrome copper cage, black bakelite base, and steel gimbles.

TYPE "90"

Precision built Moving Coil Generator provides good quality reproduction.

- Light weight, durable chrome and baked enamel metal case.
- Full tilting head.
- Excellent sensitivity.
- Robust construction.

AUSTRALIAN MADE — — FOR AUSTRALIAN CONDITIONS

Manufactured by—

ZEPHYR PRODUCTS PTY. LTD.

58 HIGH STREET, GLEN IRIS, VIC.

(Box 2, Armadale P.O., Vic.)

Phone: BL 1300

AVAILABLE FROM ALL LEADING TRADE HOUSES

A V.H.F. AUTOMATIC TUNER

BY DR. H. A. F. ROFE,* VK2HE

ONE wet Saturday afternoon, I was working on some gear in the shack with the 2 metre receiver running, prepared to talk to anyone who came up on the band, but unwilling to devote more than a few scant seconds in every five minutes to tune the receiver. By tea time I had heard and worked no one. The following week I was talking to a local fellow who said, "I called CQ several times last Saturday afternoon and could not get a contact."

On another afternoon last summer, I tuned over a quiet 6 metre band for that elusive DX at 1630 hours, then engaged in a minor task which was completed at 1646 hours. An inspired hunch prompted me to look over the band before leaving the shack. Three hours and many contacts later, after the last signal had disappeared, I retired happily to a belated evening meal. How about an automatic tuner that would draw attention to itself, like the telephone, when a signal came up?

A forward-reading v.t.v.m. type S meter using a 0-1 Ma. movement can be adjusted to give f.s.d. on an S7 to S9 signal with considerably less than a half scale reading on local noise. Could not this 1 Ma. be used to operate a relay, which, in turn, would control an electric motor and, if desired, a warning device?

Out of the junk box came a slow speed motor, a continuously-rotatable three-gang condenser and a very sensitive relay, and around these essential components was built a receiver tuning from 4 to 6 Mc.

The motor is made by a well known firm of electric clock manufacturers and designed to operate a slowly revolving demonstration turntable. This one has a speed of one revolution per five seconds and operates from 240v. a.c.

The gang condenser came out of unidentified v.h.f. gear and has a maximum capacitance of about 100 pF., ideally suited to the LC ratio of each tuned circuit for which special coils were wound to cover exactly 2 megacycles.

The relay derives from the readily obtainable BC357L and can be adjusted to operate over a wide current range from 50 microamperes to about 2 milliamperes. Its field coil has a resistance of 10,000 ohms, and, as its s.p.d.t. contacts will handle up to 10 amperes, they will easily cope with the few mills. drawn by the motor at 240v. a.c. No sparking suppression has been found necessary and the motor causes no electrical interference on the bands used.


The receiver itself is conventional average Amateur design with an r.f. stage, converter, an i.f. stage at 455 Kc., 2nd detector, a.v.c. and noise limiter, p.a., and provision for Q multiplier, b.f.o., a gated-beam n.b.f.m. discriminator and a 6 metre front end.

Referring to the circuit diagram, it will be seen that the relay field coil replaces the usual 10,000 ohms resistor

in series with the 0-1 Ma. meter. The relay is adjusted to operate at 0.75 Ma. A component in the balanced-bridge circuit, the 50,000 ohm potentiometer, is used to adjust the meter needle to zero. The 2 megohm pot. is related to the 6 megohm bleeder resistance across the a.v.c. line according to the sensitivity of the meter used and to the a.v.c. voltage available. It is the sensitivity control and is adjusted so that the highest prevailing noise peaks will not stop the motor.

The motor is geared to the gang condenser to give it a speed of one revolution per 25 seconds, during which time two megacycles are scanned twice. It can be switched off for manual tuning.

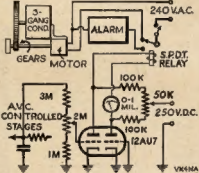The operation of the device is very smooth on the 2 metre band and at maximum usable sensitivity, that is, when the relay is just insensitive to noise, even a 5 and 7 signal will be tuned in.



The alarm could be a buzzer, bell, siren or what have you.

A fascinating application, suited to the lazy "mail reader," is when two fairly strong stations, in contact, are the sole occupants of the band. When the sensitivity control is set at the minimum level required for the weaker signal to operate the relay, the whole QSO is heard without stirring from the couch until both stations QRT. The tuner then proceeds with its job of scanning the band.

As the receiver is used in conjunction with a crystal-locked 2 metre converter, a few relevant comments would seem appropriate.

The Jones or "Shure Fire" fundamental oscillator is used with a 7.7778 Mc. crystal and a 6J6, first triode tripling and second triode section doubling. A second 6J6 is tripler and mixer. A series cascode 6BQ7 is inductively coupled to a 6AK5 r.f. stage, which is inductively coupled to the mixer.

The converter has its own power supply and is completely isolated from the h.f. receiver, except for the co-ax input lead. These precautions have completely eliminated "birdies" and "break-through" of commercials.

For 6 metre a 7.6667 Mc. crystal, multiplied six times, would bring 50 Mc. in at approximately 4 Mc. Better

still, if the tuner were designed to operate from 3 to 5 Mc., a 7.833 Mc. crystal, multiplied six times for 6 metres, and 18 times for 2 metres, would bring both 50 Mc. and 144 Mc. in at 3.002 Mc. and 3.006 Mc. respectively, the first 6J6 being used for both bands.

If we wish to combine 5 metres and 2 metres at some future date, the problem is easily solved from the equation:—

56 — $XY = 144$ — XZ

where X = fundamental crystal frequency.

Y = total crystal oscillator multiplication factor for 5 metres (6, a multiplier of 18, is convenient).

Z = total crystal oscillator multiplication factor for 2 metres (18 is selected).

hence $56 - 6X = 144 - 18X$

therefore $X = 7.3333$ Mc.

To find where 56 Mc. will appear in the h.f. spectrum:—

I.F. = sig. freq. — osc. freq.

$$= 56 - 6 \times 7.3333$$

$$= 12.0002 \text{ Mc.}$$

Checking on 144 Mc.:—

$$\text{I.F.} = 144 - 18 \times 7.3333$$

$$= 12.0006 \text{ Mc.}$$

Therefore our h.f. receiver will be required to tune from 12 Mc. to 14 or 16 Mc. to cover 2 or 4 Mc. of the 5 or 2 metre bands.

For those, who are not yet prepared to build a crystal locked converter, or prefer a generally simpler design, the electric motor could be coupled to the small split-stator condenser of a tunable oscillator for either band.

A.O.C.P. CLASS

The Victorian Division A.O.C.P. Class will commence on Thursday, 17th November, 1955. Theory is held on Monday evenings, and Morse and Regulations on Thursday evenings from 8 to 10 p.m. Persons desirous of being enrolled should communicate with the Secretary W.I.A., Victorian Division, 191 Queen Street, Melbourne (Phone FJ 8997 from 10 a.m. to 4 p.m.), or the Class Manager on either of the above evenings.




Miniwatt transistors

type 2-OC72

announce

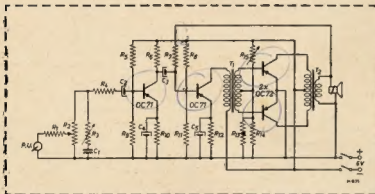for push-pull audio frequency applications



JUST RELEASED!

40-page "Miniwatt" semi-conductor booklet.

There is an excellent article on Semi-Conductors; it has application notes and full data on the "Miniwatt" range of transistors and germanium diodes.

Price 2/- (Post Free)

Applications—radio receivers, Intercom. systems, tape recorders and a host of other uses. Used singly the OC72 will give twice the power output of the OC70 or OC71.

Write for Data Sheet without obligation.

Miniwatt

DIVISION

PHILIPS ELECTRICAL INDUSTRIES PTY. LIMITED

69 Clarence St., Sydney 381-5 Murray St., Perth
590 Bourke St., Melbourne 119 Grenfell St., Adelaide
148 Edward St., Brisbane

PYL:15

Lightning Protection for the Transmitting Antenna

BY R. C. CORDERMAN, W4ZG

AN old adage says lightning never strikes twice in the same place. You may not agree with this, but if it strikes you once it won't make any difference whether you do or do not agree.

Radio Amateurs for the most part invite destruction by lightning by neglecting to provide any protection against it. The antenna usually associated with Amateur Radio transmitting equipment is most vulnerable to lightning due to its length and height. To validate your insurance, your antenna installation must comply with the National Board of Fire Underwriters Electrical Code which says:


Lightning Arrestors.—Transmitting Stations. Except where protected by a continuous metallic shield (co-ax), which is permanently and effectively grounded, or the antenna is permanently and effectively grounded, each con-

• Lightning protection for the Amateur transmitting antenna, especially when open-wire feeders are used, has been largely neglected. W4ZG points out the dangers involved and offers some simple solutions.

Penaa., an experience was observed which will be of interest in this connection. The antenna at 8XC consisted of 10 wires 800 feet long, approximately 165 feet above the ground at its centre. It ran across a gully, at the bottom of which was a mainline railroad track. When locomotives pulling heavy trains passed under the antenna, the static charge built up was sufficient to cause flash-over of an 8-inch gap. The flash


of lightning arrestors provided for residential broadcast and television antennae may be suitable for very low power installations, but where higher power is used, they are inadequate, since the radio frequency voltage on the transmission line is usually enough to cause them to operate, i.e. flash over.

During the early Thirties, advice was obtained from the Naval Research Laboratory at Washington, D.C., on a suitable grounding arrangement for lightning protection for a 1-kw. installation. It was their suggestion that a spark gap be provided between each of the two open-wire feeders and a centre contact, grounded with No. 4 or larger wire. It was recommended that $\frac{1}{2}$ " x $\frac{1}{4}$ " flat brass rod shaped as shown in Fig. 1 be used for the gaps. Each of the gaps should be set sufficiently far apart so as to prevent flash-over during normal

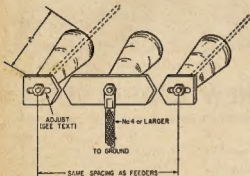

← Fig. 1—A simple lightning arrestor made from three stand-off or feed-through insulators and sections of $\frac{1}{2}$ " thick brass or copper bar.

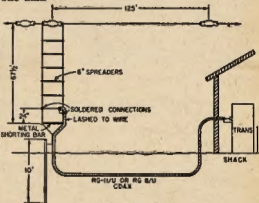→ Fig. 2—Sketch of co-axial fed grounded Zepp antenna. Adjustment is discussed in the text.



ductor of a lead-in for outdoor antenna shall be provided with a lightning arrestor or other suitable means which will drain static charges from the antenna system.

A similar requirement is applicable to a receiving antenna should it extend outside the building in which the receiving equipment is located.

Many years ago my antenna was struck by lightning. At that time, there was an insurance requirement which said that a 100-ampere switch should be used for grounding the antenna when the station was not in operation. The lightning completely destroyed most of the antenna wire, burned the wooden base of the lightning switch and burned the insulation off the No. 4 copper grounding wire between the switch and the ground stake. As the switch was in the grounded position, no damage to the house or radio equipment resulted.

Without adequate grounding, hazardous voltages can build up on an antenna due to other causes. About 1920, while attending Carnegie Tech., Pittsburgh,

repeated approximately every five seconds while the engine was immediately beneath the antenna and less frequently when it was approaching or leaving the area below the antenna.

LIGHTNING ARRESTORS

What steps should we take to protect ourselves and our equipment against these hazards? You will observe that the Electrical Code specifies that the lead-in may be a coaxial cable, the shield of which is permanently and effectively grounded. This means that a ground connection, using No. 4 wire or larger, should be made to the shield of the co-axial cable at the point where it is nearest to the ground outside of the house. If the cable can be run underground, a grounding stake should be located at the point where the cable enters the ground. The grounding stake, to be effective in soils of average conductivity, should be not less than 10 feet long, and if possible, plated with a metal which will not corrode in the local soil.

When open-wire feeders are used, a lightning arrestor is required. The type

operation of the transmitter. It was found that because of the standing waves on the open-wire line a gap of approximately $\frac{3}{16}$ inch was necessary.

This device worked very well during thunderstorms as it would start sparking intermittently when a storm was approaching. As the storms passed over the immediate area, the frequency of discharge would increase. During heavy thunderstorms, there was a steady stream of sparks at the gaps. It was possible to operate the transmitter with relatively little effect on its performance even while the static charges were jumping across the equipment, but this was seldom done because of a personal reluctance to be so close to the antenna system.

It has been my belief that a properly installed spark gap on an antenna system drains off sufficient static from the immediate area to prevent a direct hit. This view stems from the fact that during the twelve years these gaps were in use there was never an occasion when a lightning hit came closer to our house than a half block when a neighbour's house was struck. This



"THE LANDING OF CAPTAIN COOK" by PHILIP FOX. By Courtesy of the NATIONAL GALLERY OF VICTORIA.

"CAPTAIN COOK DISCOVERS NEW CONTINENT"

This was stirring news to the world of 1770, but it was three months before King George III of England heard about it.



Today, news like this would be flashed round the world by radio.

In Australia, from Cape York to Hobart, from Brisbane to Perth, radio listeners hear immediately about any dramatic national incident:

"RADIO AUSTRALIA flashes daily news around the world. Jocelyn Terry is shown here broadcasting messages from home to Australians in lonely outposts in Antarctica.

RESEARCH AND THE ELECTRICAL INDUSTRY

For years Shell scientists have worked to improve various parts of electrical equipment, such as enamelled wires, insulating materials, and resins which effectively seal radio condensers.

Shell also helped in the initial development of low vapour pressure oils, greases and sealing compounds necessary to create the required vacuum in valves. These and other problems solved in SHELL laboratories have enabled radio manufacturers to produce the high-fidelity electrical goods marketed today.



could have been a happenstance, but it is the fact, nevertheless.

In the Pennsylvania Dutch country around Lancaster and York, most barns nowadays are protected from lightning by a length of old trolley wire mounted on poles extending about 10 feet above the roof. Both ends of the wire are grounded and, so far as can be learned, no barn so protected has suffered lightning damage.

DIRECT GROUND CONNECTION

Many of our modern antennae permits relatively simple methods of direct ground connection, which do not interfere with the operation of the antenna. Rotary beams using a T or gamma match may have the centre of each of the elements, including directors and reflectors, grounded to the tower on which they are mounted. Two and six metre beams should have the supporting pole grounded. If the antenna is mounted on a wooden pole or on the top of a house, a No. 4 or larger wire should be extended from the beam to the ground, using insulators where the wire comes close to the building. The ground wire should be spaced away from metal objects such as gutters, etc., or should be solidly grounded to them. If the connection to such objects is not a good one, but is variable in resistance, it may be a source of spurious signals when excited by the transmitter. This often results in interference with your

own or your neighbours' broadcast or television reception.

For the past seven years, the antenna shown in Fig. 2 has been used at W4ZG, Winston-Salem, N.C. It gives what appears to be good lightning protection. It hasn't been hit yet. And best of all, signal reports have been more than satisfactory on power comparisons made with other stations under like conditions.

The antenna may properly be called an end-fed Zepp. Since much of the work done here is on the Tar Heel Net frequency of 3865 Kc., the antenna was cut to centre on this frequency. Operation is not confined to this frequency, however, as many contacts are made even at the high end of the band without any retuning or adjustment of either the driver or final stage tuning circuits.

The antenna is 125 feet long and the quarter wave Zepp feeders are 62½ feet long, spaced 6 inches apart. The feeders are tied together at the lower end and grounded. A metal rod 6 inches long is used as the lowest spacer. RG-11/U (72 ohm) co-ax is used to feed the Zepp feeders. The shield of the co-ax is attached to the feeder which goes to the antenna and the centre conductor goes to the other feeder which dead ends at the antenna. The point of attachment is about 24 inches from the shorting bar. The co-ax is tied to the feeder to which the shield is connected and follows it back to the shorting bar and then follows the grounded lead to the ground stake and from there runs underground to the house.

By now you are wondering why the shield is connected to the feeder which goes to the antenna instead of being attached to the feeder which dead ends. Actually, it makes no difference which way you do it, except that if you use a bridge to check the standing wave


ratio, you will have more trouble induced voltages from local broadcast stations if you reverse the connection. The feeder plus antenna picks up much more of this broadcast field voltage than the dead-ended feeder will pick up.

Another benefit from this antenna which was entirely unexpected is the reduction in harmonics reaching the antenna. At the desired frequency, the 4 feet of wire between the ends of the co-ax and the shorting bar serve as a transformer to match the impedance of the co-ax to the impedance of the operation at the desired frequencies. However, this is not the case and the higher-order harmonics are effectively suppressed. No other filter is used as W4ZG for this purpose and there is no observable interference on a television receiver connected to an antenna just 15 feet away from the Zepp feeders.

Should you wish to use this antenna on other bands, you may do so by reducing the dimensions in accordance with standard antenna formulae. The point of connection of the co-ax to the Zepp feeders is not critical and may vary somewhat under different rounding conditions. It can best be done by measuring the s.w.r. at the transmitter end of the co-ax at several different test positions, but if no bridge is available, the connection of the co-ax to the Zepp feeders may be made 24 inches from the shorting bar for 80 metres, 12 inches for 40 metres, 6 inches for 20 metres, and 3 inches for 10 metres. It is desirable that the feeder spacing be reduced at the higher frequencies as the length of the shorting bar is a factor in the impedance match.

1 For antenna systems in which the antenna and feeder lengths are the same as above in terms of wavelength.—Editor.

PREDICTION CHART FOR NOV., '55

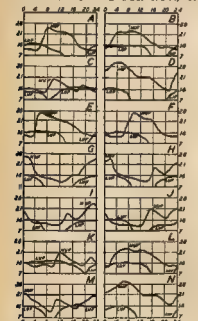

A—Eastern Aus. to West Europe—Short Route.
B—Eastern Australia to South Africa.
C—Eastern Aus. to West. Europe—Long Route.
D—Eastern Australia to Far East.
E—Eastern Australia to Mediterranean.
F—Western Australia to Western Europe.
G—Eastern Australia to North West U.S.A.
H—Western Australia to North West U.S.A.
I—Eastern Aus. to North East U.S.A.—Short Route.
J—Western Australia to North East U.S.A.
K—Eastern Aus. to North East U.S.A.—Long Route.
L—Western Australia to South Africa.
M—Eastern Australia to Central America.
N—Western Australia to Central America.

USE OF ELECTRONIC VALVES

Recently, while building a small transmitter, the valve driving the 897 would not seem to function correctly. It was one of the miniature 9-pin all glass types. Investigation showed a short between the control grid pin and another pin. This other pin was labelled, in the handbook, "IC," which we know stands for "Internally connected." It was assumed this meant connected to cathode and it had been strapped to the cathode tag on the bottom of the valve holder for convenience in wiring and layout.

On reading through the "British Standard Code of Practice on the use of Electronic Valves" it is learned that any pin labelled "IC" should be severely left alone. This pin, or any pin labelled "IC" may be connected anywhere or to any other electrode in the valve without the connection being specified, in fact, it states that valves of the same type, but of different manufacture, will most likely be connected differently internally. It even states that valves from the same manufacturer may be connected differently, depending on when they were made.

There is a lot of interesting "dope" in this book for those who employ a large number of valves and for Amateurs, too. For instance, it recommends that the cathode to heater capacity never be

put across a tuned circuit. This is quite common practice with Amateurs and probably accounts for some of the unsatisfactory signals.

It further recommends that cathode keying should not be so arranged as to leave the cathode "in the air" when the key is up. A maximum resistance of 0.25 megohm should be connected between cathode and heater. Similarly with screen grid keying. This, of course, is not generally used anyway as it does not always kill the signal when the key is up.

The book has plenty to say about over-running valves—which in any language is to be deprecated. It is well known that the envelope should be kept cool by either plenty of natural air circulation or forced draft. Since reading this, a small fan has been arranged to blow the final. It is probably not so well known that it does not matter much—within reason—what the ambient temperature of air is that circulates around and past the valve, that is, tropics or the North Pole, as long as there is sufficient air.

One final tip. It is bad practice to use spare valve holder contact lugs as anchoring points in circuit wiring. Sometimes the pins go inside the valve and although not connected, the application of h.t. can upset the functioning of the valve.

—Reprinted from "R.S.C. Bulletin," March-April, 1955.

ATI-TVI FILTERS FOR THE AMATEUR TRANSMITTER

BY H. F. RUCKERT,* VK2AOU

cannot be said often enough that we must first build the transmitter with as low harmonic power output as possible and the chassis and shielding cabinet must be free of r.f. or the best low-pass antenna filter and mains filter will be of very little help. The filter will not cure all ills we may have built into our transmitter. How this cure can be effected, before we use filters, was described by the writer in an earlier issue of "Amateur Radio." The filter on our transmitter will not offset the design features the neighbours' t.v. receiver may lack, making it hard to prevent t.v.i.

The following description of a typical low-pass filter shows how we can plan, calculate, build, test and use these filters. In spite of a few formulae there are no more mathematics involved than our children learn now at school. If you know how to use a slide rule and a grid dip meter, it will not take you longer than 20 minutes to calculate the filter components and frequencies, and the aligning can be done in a further 20 minutes.

Fig. 1 shows how a low-pass filter can be inserted between the pi-filter network final of our transmitter and the antenna coupler.

The pi network helps to reduce harmonic output, so does the antenna coupler, too. The coupler permits us to use any aerial we may have and still have the benefit of the filter. The filter can only work efficiently if we have a specified impedance on both filter terminals. Of course there must be a low standing wave ratio of less than 2:1 or we will overload the filter components, causing their failure or excessive losses.

The filter we will describe now can be placed anywhere in a 70 ohm flat co-ax line, even 52 ohm cable will not make much difference to the filter performance.

If we do not use the antenna coupler we can go directly from the filter output terminal to the flat line (52 to 70 ohm cable), which may be twin lead or co-ax cable. If a pi-network tank is not used a link coil has to be placed at the filter input and coupled to the tank circuit. The method shown in Fig. 1 has several advantages over other possibilities as outlined above, because any band below the filter cut-off frequency and any aerial may be used regardless of the type of feeder we may have.

Fig. 2 is the attenuation curve we can expect with the type of filter we are planning now.

The h.f. DX hunter will be interested in suppressing the 3rd harmonic of 14 Mc., the 2nd harmonic of 21 Mc., and of course any higher harmonic frequency. Therefore he does not want any attenuation below 30.5 Mc., but he wants full attenuation at 41 Mc. and higher.

The v.h.f. Amateur wishes to get 60 Mc. and 148 Mc. without losses, but the

3rd harmonic of 60 Mc. should be attenuated and also any harmonic of higher order.

Attenuation of about 60 db. (1000:1) of the undesired harmonic between the input and output terminals of the filter is usually regarded as sufficient. A filter with more sections and a higher theoretical attenuation, may not pay because the transmitter chassis may not be free enough of r.f., including harmonics, that may be radiated to the mains, water pipes, gutter, etc.

Fig. 3 shows the low-pass filter, now an integral part of practically any Amateur transmitter, home-built or manufactured, in U.S.A. at the present time.

The filter starts, from left to right, with an M-derived section, there is a constant K-pi section in the middle, and again symmetrically an M-derived end section.

The formulae we find in the A.R.R.L. Handbook, and in other text books, are always correct for a chain of similar filter sections. If we use only one of each, we have to change the formulae as follows:

$$L1 = m \times Lk$$

$$L2 = \frac{1 - m^2}{2m} \times Lk$$

$$m = \sqrt{1 - \left(\frac{fc}{fo}\right)^2}$$

L1, L2, and Lk—See Fig. 3.

m = values between 6 and 8 (often used), m = 6.5 in our example.

fc = the cut-off frequency where the attenuation begins to rise steeply (in c.p.s.).

fo = a high frequency with extremely great attenuation (in c.p.s.).

$$Lk = \frac{R}{\pi \times fc}$$

$$Ck = \frac{1}{\pi \times fc \times R}$$

$$C2 = \frac{1}{2} m Ck$$

where—

Lk is in henries.

Ck, C2 is in farads.

R in ohms.

fc in c.p.s.

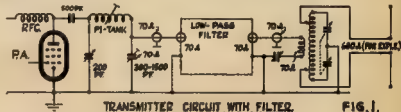


FIG. 1.


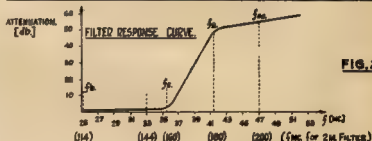


FIG. 2.

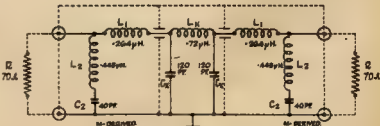

COMPONENTS OF THE FILTER

FIG. 3.

* 25 Berrille Road, Beverly Hills, N.S.W.

R is the input and output impedance, 52 or 70 ohms for example, depending on the type of cable and feeder used.

C2 and Ck are filter capacitors, see Fig. 3.


We get so far if we study the Handbook, but we would like to know how to find fa where the attenuation has the first high value. Making a filter with the formulae given above and m near 6.5, we will find that:

$$fa = \frac{1}{2} (fc + fc)$$

when we check the completed filter with the grid dip meter. Since we like to determine fa first and calculate fc we say:

$$fc = 2 fa - fa$$

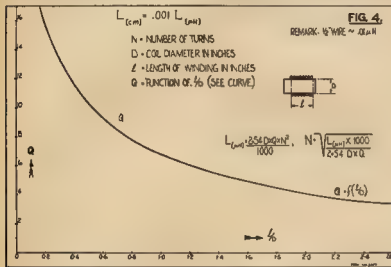With these formulae we can calculate all filter components. We only need now to find out the frequency fb to be able to tune the constant K section of the filter.



COIL TABLE			
	Coil Diam.	Coil Leng.	Turns
L1	1/2"	3"	6.5
L2	1/2"	3"	9
Lk	1/2"	1 1/2"	13

No. 14 to 18 s.w.g. wire.

The capacitors C2 and Ck are preferably NPO (temperature coefficient of the capacity zero) ceramic disc type capacitors with a power factor better than 0.05%. For Ck tubular stand-off capacitors of NPO dielectric are very easy to mount. With a standing wave ratio on the co-ax line where the filter is installed of not more than 1.3:1, receiver type capacitors are satisfactory for transmitter of several 100 watts input.

ALIGNING FILTER

The alignment of the filter is no problem with a calibrated grid dip meter using the following procedure:

high we get holes in the attenuation curve at high frequencies which may make the filter useless.

3. The third step is to disconnect the already tuned coils from Lk and use only the components as shown in Fig. 8.

By changing the spacing of coil Lk we can tune this section to fb = 25 to 28 Mc. Comparing measurement and calculations we will see that they agree even at these frequencies up to within 10%, proving that theory and practice must not always be hopelessly apart.

We now connect a three-turn link to the filter input and the Ge diode r.f. voltmeter (calibration is not required) to the output terminals of the filter. Also parallel to the terminals we have to put 50 ohm low inductive carbon resistors which will have a somewhat high impedance depending on their



INDUSTRIAL ELECTRONICS

offers young men of stamina, integrity and skill a wide field in which to exercise their talents.

- Electronic Motor Controls.
- Electronic Timing.
- Electronic Growth Control.
- R.F. Welding.
- Process Control.
- Automotons.

If YOU are interested write or phone

GLORAD ENGINEERING SERVICES

291a TOORONGA RD., S.E.6

MALVERN, VICTORIA

Phone: BY 3774

$$fb = \sqrt{\frac{25.33}{Lk \times \frac{1}{2} Ck}}$$

where f is in Mc, L in uH., C in pF.

With m values of about 6.5, fb will be about as follows:

$$fb = \frac{fc + fa}{3.2}$$

We know now all C and L values and the three frequencies, the filter sections will have to be tuned to. We have also determined the frequency where we can expect full attenuation (fa).

Fig. 4 gives us the formula and the curve for the coil form factor [Q = f (L/D)] and it is only a matter of minutes to calculate the coil turns and dimensions if we have a slide rule. All explanations are on that graph.

For our special example a coil table may be given with the dimensions of the coils used in the filter after these had been correctly tuned so that any lead inductances are already taken into account, as these do not appear in the coil calculations. Half an inch of wire represents about 0.01 uH.

Fig. 5 demonstrates how the g.d. meter can be coupled with a single loop link to the small coils in their shielding compartments. For aligning we do not need the three turn link on the left side, the two 50 to 70 ohm matching resistors nor the Ge diode r.f. voltmeter on the right side of the circuit.

1. The first step is to separate L2 on each filter end from the rest of the circuit and we have to make a very short short-circuit connection at the co-ax cable connectors. This is shown in detail on Fig. 8. With the g.d. meter we check the tuning of L2 to fa = 47 Mc. by varying the spacing of the coil turns. This is done on both filter ends with the L2 coils.

2. The second step is to wire the two filter sections as shown in Fig. 7, which means that Lk is removed as well as the short over the co-ax terminals. As with the g.d. meter coupled to the L1 coils (one after the other), we adjust only L1 to the cut-off frequency fc = 35.5 Mc. by spacing the coil turns correctly. If we tune L1 to a too low frequency we get attenuation in the 28 Mc. band. If we tune this coil too

construction. Coupling the g.d. meter now direct to the three-turn link and tuning from 3.5 Mc. up to 30 Mc. will not show any attenuation at all if we take into account that our g.d. meter does not give a uniform output of r.f. over the whole range. There is a very slight attenuation at 30.5 Mc. of less than 1 db. Three db. will be observed at 35.5 Mc., and now comes a steep drop in reading of the output meter. At 40.8 Mc. we can increase the coupling to the g.d. meter and by carefully tuning the generator we will see that the sharp peak of high attenuation is near 41 Mc. Even the tightest coupling to the g.d. meter will not give any output voltage reading. This shows that the attenuation must be at least 40 db. and 50 or more db. can be expected.

It is a good idea to tune up to 200 Mc. to ascertain if there are any holes in the attenuation curve caused by self resonance of capacitors with their leads. Re-arranging of components will help.

The low-pass filter is now ready to be placed in the transmitter as indicated by Fig. 1. A test run with different transmitter output frequencies will

prove that there is no attenuation on any band which may effect the DX efficiency.

The writer had a small electric globe parallel to the dummy antenna and was checking the output, with or without the filter, maintaining the same drive and input to the final, with a photo electric exposure meter. There was no detectable difference.

After running the transmitter with full power for 30 minutes with the filter inserted, the lid was opened, and only the coils showed a very slight increase in temperature of not more than 30°F. whilst the ceramic capacitors remained cool.

If our transmitter was shielded, as outlined before, the rest of the radiated harmonic energy should now be attenuated by a ratio of 300 or 1000 to 1, which should be enough in most cases.

These filters may be built for other impedances or symmetrically as well or with more constant K = sections.

Fig. 5 shows the layout of the components. It is important that C2 and L2 are soldered as closely as possible

to the co-ax connectors. L2 should be placed at right angles to L1 to reduce magnetic coupling.

The writer used, as shielding for the filter, three paper capacitor cans which were soldered together to give the right size of $2 \times 2 \times 7\frac{1}{2}$ inches. Ceramic feed-through insulators were used between L1 and L2. The lid should have good electrical contact to the walls between the sections and all the way around the edge and should be bent over the cans. At least six screws should hold the lid in place. The filter box must have a very good contact with the r.f.-free transmitter chassis.

A MAINS LINE FILTER

The now described untuned filter (Fig. 9) is mainly used to prevent r.f. from the transmitter power supplies escaping along the mains cable. Similar filters are recommended for use in all cases where r.f. may try to leave the shielded h.f. stages via the cables going to the power supplies.

With equal results we can, and should, filter microphone, morse key, monitor or other control cables coming from the transmitter. For the microphone cable we would have to use 100 pF. capacitors to avoid by-passing the a.f.

There is not much to say about the construction of these filters. The coil or coils are wound on $\frac{1}{4}$ inch formers which could be bakelite tubes. The winding is 3 inches long, using No. 16 or 18 gauge copper enamelled wire.

It is important to use only co-axial capacitors because no other style will have short enough leads, not even H-K ceramic discs, and therefore a low enough inductance to be effective at the frequencies which must be by-passed.

Ceramic button type capacitors of about 2000 pF. capacity, which are directly soldered to the shielding can, are ideal. The coil leads are soldered to the centre rivet. H-K ceramic capacitors can now be made to take any d.c. or 50 c.p.s. voltage we may have in our Amateur transmitters. Tubular feed-through capacitors of sufficient wall thickness to work safely can be used too.



Even a t.v. receiver advertised to be "the world's best receiver" may lack front end selectivity and a high-pass filter could help. This type of filter may be described later.

AWARDS FOR TECHNICAL ARTICLES


Following the announcement in the November, 1954, issue of "A.R." Awards for Technical Articles have been made to: N. L. Southwell, VK2ZF, "Wide Band Audio Phase Shift Networks," June; J. R. C. Miller, VK2ANF, "The New Look in Frequency Modulation," October; G. M. Bowen, VK5XU, "Twin Lead Sprigs," April.

DO NOT FORGET!

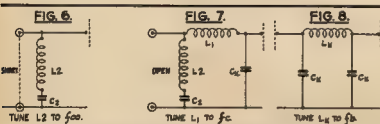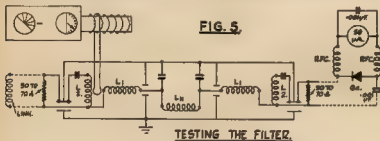The closing date for copy for the January issue is 2nd December.




HOW TO TUNE THE FILTER SECTIONS.

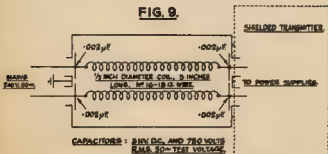

MAINS LINE FILTER

RADIOTRON POWER VALVES

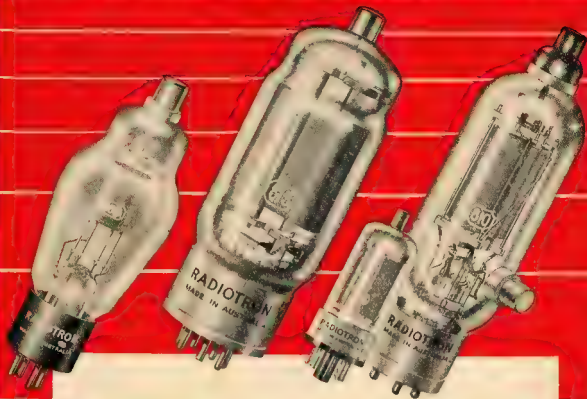

Today's high standards of radio performance are dependant upon the use of first quality components.

Radiotron valves are manufactured to exacting standards which ensure you of the ultimate in performance at all times.

Be sure of the quality and consistency of your signals by using Radiotron Power Valves.

Important: When ordering valves, be sure to mention "Amateur Radio" so that priority can be given to your order.



RADIOTRON

AMALGAMATED WIRELESS VALVE CO. PTY. LTD.

Ross Hull Memorial V.h.f. Contest, 1955-56

RULES

1. The Contest will take place in the 50-54 Mc., 56-80 Mc., 144-148 Mc., and 288-296 Mc. bands, and will commence at 0001 hours E.A.S.T. on 1st December, 1955, and will continue until 2359 hours E.A.S.T., 31st January, 1956. Interstate, Intrastate and Overseas contacts are allowed. Cross-band working is not allowed. L.A.O.C.P. licensees are encouraged to work on the 144 Mc. and 288 Mc. bands.

2. Only one contact on each band with any one station, per twenty-four hours, commencing midnight E.A.S.T., to count for scoring purposes.

3. Exchange of a serial number will constitute a contact.

4. The serial number of five or six figures will be made up of the RS (telephony) or RST (telegraphy) report plus three figures which may commence with any number between 001 and 100 for the first contact and which must increase in value by one for each successive contact, e.g. if the number chosen for the first contact is 050, then the number for the second contact must be 051, for the third 052, and so on. If any contestant reaches 999, then he must start again 001, and continue as above.

5. Scoring.—Points allotted, apply to each band worked.

Interstate and Overseas Contacts: 5 points for the first contact with any particular station, 4 points for the second, and so on to the fifth contact for 1 point, after which no more scoring

contacts with that particular station can be made on that band, for the duration of the Contest; e.g. VK5ABC may work VK2XYZ five times on each of the four bands, for a total of 20 contacts.

Intrastate Contacts (for VK Call Areas only).

(i) Five points for the first contact with any particular station, four points for the second and so on to the fifth contact for one point, after which no more scoring contacts with that particular station can be made on that band for the duration of the Contest.

(ii) Stations located beyond a radius of 100 miles of any Capital City (Federal Capital excepted) will double their score for ALL contacts; e.g. VK3ABC (Mildura) works VK3XYZ (Melbourne) for the first contact: VK3ABC scores 10 points, while VK3XYZ scores 5 points. If VK3ABC works VK3PQR at Red Cliffs, both score 10 points for the first contact.

6. Logs shall contain the following information: Date, time (E.A.S.T.), band, call of station contacted, serial number sent, serial number received, points claimed for the contact, and at the foot of each page the total points claimed; and at the end, the grand total.

Logs shall be signed by the competitor, together with a declaration to the effect that the station was operated strictly in accordance with the rules, and spirit of the Contest. The decision

of the Federal Contest Committee shall be final and binding.

Logs must be received by the Federal Contest Committee, Box 1234E, G.P.O., Adelaide, South Australia, not later than 1st March, 1956.

7. Entries will be accepted from all States of the Commonwealth and Districts of New Zealand. Check logs from other countries would be appreciated by the Contest Committee.

8. The regulations governing the control of Amateur Radio in each contestant's country must be observed.

9. Awards: (a) For the purpose of Awards, Northern Territory will count as a separate call area.

(b) The outright winner of the Contest within the Commonwealth of Australia will receive an appropriately inscribed Certificate.

The top financial member of the W.I.A. will hold the Ross A. Hull Memorial Trophy for a period, and in addition will receive an appropriately inscribed photograph of the Trophy.

(c) The highest scorer in each call area in Australia and New Zealand will be awarded a Certificate. The Federal Contest Committee reserves the right to make any additional Awards.

(d) A Certificate will be awarded to the L.A.O.C.P. licensee who gains the highest score in each call area. (Operation must be confined to the 144 Mc. and 288 Mc. bands with A3 emission, to conform with the Departmental Regulations.)

10. The decision of the Federal Contest Committee will be final and binding upon all matters pertaining to this Contest.

SPECIAL

BRIGHT STAR RADIO are pleased to announce an addition to their line of Crystals. We are now manufacturing—

VACUUM MOUNTED CRYSTALS

for general communication frequencies in the range 3 to 14 Mc.

Higher frequencies can be supplied.

ADVANTAGES OF THIS TYPE—

- (1) Approximately three times the activity of normal plated crystal due to the absence of air damping.
- (2) Better frequency stability due to the absence of air friction.
- (3) Plating cannot deteriorate with time and cause frequency shift.
- (4) Two or more crystals can be mounted in the one envelope and thus save space.

Price depends on the tolerance and frequency required, and will be quoted upon request.

BRIGHT STAR CRYSTALS may be obtained from the following Interstate firms: Messrs. A. E. Harrold, 123 Charlotte St., Brisbane; Gerard & Goodman Ltd., 192-196 Rundle St., Adelaide; A. G. Healing Ltd., 151 Pirie St., Adelaide; Atkins (W.A.) Ltd., 894 Hay St., Perth; Lawrence & Hanson Electrical Pty. Ltd., 120 Collins St., Hobart; Collins Radio, 409 Lonsdale St., Melbourne; Prices Radio, 5-6 Angel Place, Sydney.

BRIGHT STAR RADIO

46 EASTGATE ST., OAKLEIGH, S.E.12

UM 3387

OLYMPIC GAMES COMMUNICATION DEMONSTRATION

Following an approach to the W.I.A. by the Olympic Games authorities, the 2 metre gang was organised by Len Moncur, 3LN, to demonstrate the possibilities of conducting radio communication between the Melbourne Cricket Ground and various spots along the route of the marathon walking events of the forthcoming Olympic Games. The route is to Springvale via Dandenong Road and return to the M.C.G.

The basic requirement was for a 144 Mc. base station set up at the M.C.G. working to mobiles along the route. Fast experience of field days, mobile tests, fox hunts, etc., gave full support to the suitability of v.h.f. for the job. After several discussions at the V.h.f. Group meetings, it was decided that, at least for this test, a better base station location than the M.C.G. site would not be amiss, and Alf 3IE, checking with a contour map, came up with the suggestion of the Malvern Town Hall clock tower, this being not only suitably situated, but also at considerable altitude. Alf arranged access to the building and our thanks are due to him and to those who gave the necessary permission.

Being now assured of good signals from the mobiles, it was deemed that it would be a simple matter to relay two way via radio link direct to the M.C.G. if necessary.

3IE and 3YS, armed with a 2 metre transmitter and receiver and a 5 over 5 portable beam, set up the base station in the small room above the clock, with the beam mounted on the open top landing. The wonderful view obtainable from the tower provided compensation for the long climb and visual justification for the selection of the site. The weight of the equipment and general set-up of the stairs made it necessary to remove the various sections from the transmitter and receiver rack and carry them up piece by piece and reassemble. The convenient construction of 3TO's rig made this a relatively easy

matter, and by 12 noon the base station was in operation. 3ZBJ and friend, John Hamilton, provided a test contact, and responded willingly to a request for assistance in the afternoon when the gear had to be dismantled and removed.

At 2.30 p.m. four mobiles, 3VZ, 3ALY, 3ZBU and 3APB, met two officials of the Olympic Games Athletic Committee at the M.C.G. 3LN was unable to participate due to a bereavement in his family. It was arranged that one of the officials would accompany 3VZ on a tour of the route, followed at intervals by 3ZBU and 3APB; all to maintain contact with the base control station operated by 3IE. 3ALY remained at the M.C.G. to enable the other official to hear the base station contacting the mobiles with their position reports. 3ALY later moved off along the route, and all cars maintained contact with the base station throughout the test, with excellent signals both ways.

On the return journey, further tests were made including working between the cars. Tests from so-called "dead spots" were quite successful.

All gathered at the Town Hall for a discussion and inspection of the base station site. Officials were extremely pleased and enthusiastic with the results and voted it the best and most successful demonstration they had witnessed. Their congratulations to the Institute were very encouraging and provided compensation for the members' efforts. We, in turn, thank all those who participated so enthusiastically. It is hoped that outside interests will not preclude the Institute from putting its efforts and results into practice.

The advisability of all mobiles working on a spot frequency for such a job was evident, but lack of time did not permit this to be arranged. The above account provides another indication that the W.I.A., when faced with a job, can, and will, do it with the co-operation of its members.

VK3 AWARD FOR 100 V.H.F. CONTACTS

Since this award was originally announced in 1951, three of these certificates have been issued, firstly to Jim 3ABA, then to Col 3FO and Fred 3YS. This award is available to those in VK3 who make 100 or more contacts above 100 Mc.

The rules are as follows:—

(1) Awarded to those VK3 Amateurs holding either the limited or the full license, who submit evidence of having contacted two-way, at least 100 other stations on Amateur bands above 100 Mc., during from 1st January, 1948.

(2) Confirmations to show the usual QSL information including call sign and location, date contact was made, band used and report.

(3) All authorised bands above 100 Mc. and any authorised type of emission may be used, provided always that the Amateur Regulations are observed.

(4) The claimant licensee may have operated anywhere within Victoria and

either he or the station worked may have operated mobile, portable or fixed or may have changed address.

(5) Only one contact per licensee may be claimed regardless of band used or method or location.

(6) Claims to be submitted in writing to Secretary, Vic. Div., together with a legibly written list of the confirmations submitted. The confirmations should be forwarded by registered mail and return postage should accompany the application.

(7) An attractive certificate to be awarded to each successful applicant.

(8) The V.h.f. Group reserves the right to modify the rules if necessary (subject to sanction of Vic. Division Council).

(9) In case of any dispute concerning a claim, the scrutineers (at present the Chairman and Secretary of the V.h.f. Group) decision to be accepted as final.

JANUARY ISSUE

This time every year a plea is made to Advertisers and Contributors to forward copy early for the January issue.

To explain once again, as the printers close down for annual holidays from just before Xmas until the middle of January, it is necessary, if the magazine is to be posted to you on the 1st of January, for the magazine to be printed before Xmas.

Therefore it is requested that material for the January issue must reach 181 Queen Street, by the SECOND OF DECEMBER.

Your co-operation in this matter will be appreciated.—Editor.

Low Drift Crystals FOR AMATEUR BANDS

ACCURACY 0.02% OF
STATED FREQUENCY

3.5 Mc. and 7 Mc.

Unmounted £2 0 0

Mounted £2 10 0

12.5 and 14 Mc. Fundamental
Crystals, "Low Drift,"
Mounted only, £5.

THESE PRICES DO NOT
INCLUDE SALES TAX.

Spot Frequency Crystals
Prices on Application.

Regrinds £1 0 0

MAXWELL HOWDEN
15 CLAREMONT CRES.,
CANTERBURY, E.7,
VICTORIA

"ACOS" CRYSTAL MICROPHONES and MICROPHONE INSERTS

A Complete Range For Every Purpose

DESK OR HAND MICROPHONE

MIC 36



£6/18/6

Housed in attractive plastic case, this Microphone is ideal for home recording and public address, etc. Response unexcelled for its size and price. The performance is not affected by vibration, shock or low frequency wind noise. Omni-directional frequency response substantially flat from 30 to 7000 c.p.s. Recommended load resistance not less than 1 megohm dependent on low frequency response. Can be supplied complete with switch and floor stand adaptor as required at a small extra cost.

HIGH QUALITY MICROPHONE

Designed to meet even the most exacting requirements, this Microphone incorporates the world famous floating crystal sound cell construction. Its special characteristics are that its fine performance is not affected by vibration or shock. The fidelity is not impaired by low frequency wind noise.

SPECIFICATION

Recommended load resistance—not less than 1 megohm.
Output level —55 db ref. 1 volt/dyne/cm².
Frequency response—substantially flat from 30 c.p.s. to 10,000 c.p.s.
Directivity—non-directional.
Size—2½" spherical diameter.
Connection—Standard International 3-pin.

MIC 16



£24/19/6

GENERAL PURPOSE MICROPHONE

MIC 35



£2/15/-

substantially flat response from 50 to 5000 c.p.s.

SPECIFICATION

Output level: —55 db ref. 1 volt/dyne/cm².
Cable—approx. 4 ft. of co-axial supplied.
Weight—6 ozs. unpacked, 7 ozs. packed.
Dimensions—microphone only 2½" x 2½" x ¾"

TABLE AND STAND MICROPHONE

This omni-directional Microphone is robust in construction, with a pleasing appearance. Vibration, shock or low frequency wind noise will not affect the performance. The low frequency cut-off is dependent on the load resistance. The cut-off is given by the quotation, $F = 80 + R$, where $F = \text{c.p.s.}$, $R = \text{megohms}$. An adaptor (floor mounting) is available at low extra cost.

SPECIFICATION

Output level = —50 db ref. 1 volt/dyne/cm².
Output impedance—equivalent to approximately 0.002 uF. (0.8 megohm at 100 cycles).
Frequency response—substantially flat from 40 to 6000 c.p.s.
Recommended load resistance—not less than 1 megohm, dependent on low frequency response.

MIC 22



£9/18/6

LAPEL MICROPHONE

MIC 28



£5/19/6

Designed to give freedom of movement, this Microphone is small and non-directional. Housed in a soft moulded rubber case, which gives protection against shock, it is provided with a pin at the rear of the case for pinning to the lapel.

SPECIFICATION

Output level—approx. —55 db ref. 1 volt/dyne/cm².
Recommended load resistance—5 megohms.
Frequency response—level throughout the whole of the audible spectrum.
Capacity—0.0015 uF. at 1000 c.p.s.
Impedance—100,000 ohms at 1000 c.p.s.
Cord—5 ft. shielded cable.
Size—1-9/16" wide x 2¼" long x ¼" thick.

HAND OR DESK MICROPHONE

MIC 33



£6/18/6

This Microphone has been designed for the high quality public address and home recording field. High sensitivity and flat characteristics are obtained by a specially designed acoustic filter. Housed in an attractive plastic case with an unexcelled response for its size and price. Unaffected by vibration, shock or low frequency wind noise. Omni-directional frequency response substantially flat from 30 to 7000 c.p.s.

MICROPHONE INSERTS

CRYSTAL MICROPHONE INSERTS

These inserts are available in varying sizes ranging from as small as 15/16" square to 1-13/16" round, with various thicknesses from 7/32" to 9/16". Suitable for every purpose such as hearing aids, public address, tape recording, amateur broadcasting, etc., they have responses from 2250 c.p.s. to 3500 c.p.s. at 5 db to 30 db. Insert can be supplied with or without 10 meg. resistor as required.

MIC 19/4 and MIC 32 Inserts, £2/15/6; all others, £1/19/6.

MICROPHONE INSERTS



(MIC 23 Illustrated)



(MIC 32 Illustrated)

EXCLUSIVE AGENTS:

AMPLION (A'SIA) PTY. LTD.

SYDNEY, AUSTRALIA

The Widely Acclaimed MULLARD "5-10"

High Quality Low Cost Amplifier

Comes to Australia!

The need for a well designed, low cost, high quality amplifier is reflected by the already unprecedented wide acceptance of the Mullard 5-10 amplifier. The popularity of the design, both in England and America, has resulted in the amplifier being now available in many kits forms—even a printed circuit version.

A brief specification of the amplifier is as follows:—

Power Output: Rated output 10W. Max. output 12.13W.
Total Harmonic Distortion: The total harmonic distortion is less than 0.4% at 40 c/s measured for 10W, output with normal loading and sine wave input.
Hum and Noise: —71db relative to —0W
Frequency Response: ± 0.5 db 10 c/s to 20,000 c/s.
Sensitivity: An input of 50mV to the first valve gives 10W, output. This output power is produced by an input of 400mV to the tone control circuit.
Treble Control: Continuously variable control of treble from +10db to —0db at 0.000 c/s.
Bass Control: Continuously variable control of bass from +1 db to —5db at 20 c/s.

Companion unit to the Mullard 5-10 amplifier is the AG2002 low cost, 3-speed player unit. This world-wide popular high quality player is now made in Australia and features an extremely low rumble level yet high torque. Standard equipment is a dual styli head but individual microgroove and 78 r.p.m. plug-in heads giving an even wider range are available. For the most fastidious, there is a microgroove head with a diamond stylus.

Designed by valve applications engineers for quality performance at low cost, the construction of the amplifier is fully described in Mullard publication MV8104 now available in your State for 3/9 (post-paid, 4/3).* This booklet also contains details of the AG2002 player, equalisation networks and an outstanding horn-type loud speaker enclosure. The latter enables the use of low-cost speakers — surprising performance from the inexpensive, locally made speakers recommended in the Australian section of the booklet.


*Mullard does not supply the assembled amplifier or a kitset, but the complete 5-10 amplifier kit including an approved output transformer can be obtained from Electronic Products, Box 28, Post Office, Punchbowl, New South Wales.




MULLARD-AUSTRALIA PTY. LTD.
 35-43 Clarence Street, Sydney. BX 2006
 592 Bourke Street, Melbourne. MU 2366

Associated with
 Mullard Ltd., London Mullard Overseas Ltd.

DISTRIBUTORS—N.S.W.: Bloch & Gerber Ltd., 46-48 York St., Sydney, Martin de Launay Pty. Ltd., 289 Clarence St., Sydney, Martin de Launay Pty. Ltd., Cor King & Darby Sts., Newcastle, Lawrence & Hanson Electrical Pty. Ltd., 33 York St., Sydney, Vic.: Howard Electronics & Radio Co., Vess St., Richmond, Melbourne. **Qld:** E. Marlin Pty. Ltd., 35 Charlotte St., Brisbane, Burns Philp & Co. Ltd., Box 2210 G.P.O., Brisbane. **S.A.:** Woolford & Crabbe Ltd., 18 Chesser St., Adelaide, Gerard & Goodman Ltd., 192/196 Rundle St., Adelaide, Harris, Scarle Ltd., 74 Grenfell St., Adelaide. **W.A.:** Harris, Scarle & Sanderson Ltd., 691 Hay St., Perth.

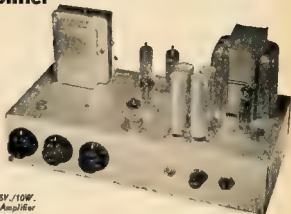

5V.10W.
Amplifier

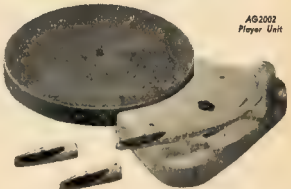

AG2002
Player Unit



Mullard
Publication
MV8104

OE*, PJZAN*, LA* VR2* VS6*, I19₁, XEIMJ*

3.5 Mo. Again, conditions were quite reliable as far as times of break-throughs were concerned. Signals were best during the following periods: 2000-2100x for Europe, and 0730-1200x for North America, with the possibility of break-throughs from other parts of the American continents.

7 Mc. The interference from broadcast and other commercial stations in the exclusive Amateur band 7000-7100 Mc. has now reached such a calamitous degree that the all-important Amateur propagation observations are extremely difficult.

Judging by the Amateur activity in the narrow spots between interfering transmissions, this is the report for the month: Europe via short route around 1900-2130z, and 0800-0800z over the long path, North and South America between 0800z and 1400z, and the Far East and the Pacific Islands around 0800z and 1400z.

14 Me. Conditions were reasonably good and reliable during the month of September. Good openings took place to all continents of the world. Stations in North America were present around the clock, while South American conditions peaked between 8300 and 8900z. With some occasional break-throughs over the short path, European were best over the long path (8500-9000z). Africa could also be worked during that period.

21 Me.: Here conditions were good to very good when an opening occurred. Normally, conditions followed the pattern typical for this band. The American continents around 2300-0400z, with Europe between 1900z and 2300z. The Far East and the Pacific Islands were likely to be workable at any time between 2300z and 1200z.

27 and 28 Mo.. These bands showed a marked improvement during the month, as was to be expected. Good openings were reported to North and Central America.

Can you listen on 7 Mc? OK, let's have your report on anything you can identify between 7000 and 7100 Kc. Note the time of reception and the call or name of any non-Amateur station operating in that range! **Old-timers and short wave listeners alike, this is a job for all of us! After all, it is our 7 Mc. band!**

It is reported that **ON4QX**, at present in Japan, will soon be active from **AC4 land**. (from N.C.D.X.C.)

According to ZS6AJH, the only Z89 station now active is Z89BD (14 Mc. phone). (from W6YY)

Further details are now available on **ZD9AD**, Gough Island. This is a sub-Antarctic island about 280 miles south-south-east of Tristan da Cunha. The operation is intended to be on all bands with possible emphasis on 21 Mc. c.w. and phone. According to the itinerary, the station should now be in operation and remain active for six months. (from 3YS)

The five stations presently active from Martinique are FM7WD, FM7WF, FM7WH, FM7WP, and FM7WQ. (from W6YY)

VS2DQ expects to go to Christmas Island (ZC9). (from N.C.D.X.C.)

FW8AB, Wallis Is., is still available on 14 Mc. c.w. The best time is apparently between 0430z and 0455z. (from

Well known s.w.I. and contributor, Jim Hunt, presently in England, mentions these VK3 signals as being among the best on phone over there: VKs 3AD, 3QK, 3VA, 3XI, 3ZL, 3ACE and 3AHC on 14 Mc. and 3ADP on 21 Mc. (from 3ZBO).

• Hans J. Albrecht, 10 Belgravia Ave., Box Hill North, E.12, Vic.
• Call signs and prefixes worked.
• — zero time—G.M.T.

(from W6YY, N.C.D.X.C., VKs 3PG, 5WO,
1LZ, and Rod de Belfour)
HKPC—C/o. Apartado Aereo 3418, Bogota,
Colombia.
VP8BD—Via International Short Wave League,
London, England.

FIMXX-Via R.E.F.
 CHCSW-C/o. Airport, Goa, Portuguese India.
 FIMBR-Box 730, Tananarive, Madagascar.
 ZPSIF-C/o. American Embassy, Asuncion.
 ETSLB Box 114, Addis Ababa, Ethiopia.
 ZSRL-Via ZS1PD
 SVQWS-A.P.O. 206, New York (WYPCR).

5A1TJ—A.P.O., 231, New York.
HB1KU/HE—Via HK9KU
5A1TL—Box 372, Tripoli, Libya.
VR3B—Deane Laws, C/o Cable and Wireless,
Fanning Island, via Suva.

ACTIVITIES

2.5 Ms.: John SEC reports Ws. Jack 62J heard ZSSPM on phone (August). Eric BEMS 195 adds W7 and FKAR/MM. Dave Jenkin heard W1, W3, W7 and S. SANE worked W3 and W9.

7 Mc.: Laurie LAMB heads the list with YVIAD* and VS8CG, FIRAC, VS8CQ, ZS8OX on c.w., and HP3FL* and JALALL on phone. Noel SZO heard HP2, while Frank SZU reports JA1, JA3, JA5, HP3FL, HR1, KE1LN, HC1FS.

Kel ZAEF heard FMTWQ. Les iXJ spoke to
 JA1AMZ and a series of Ws. Jack 8EJ
 worked on c.w. JASCP. JAAZE. VETKX
 VP0GT. VS3ET. DMBX. ZS8SF. Z3SPK.
 ZS3QD. and on phone Z58JM. Tim ZBZO
 listed JA and KH6. BE8BS reports FKUAR/
 NMJ (on phone) and DL4ZC. DUTSV. EAICS.
 YV10V. G5VW. ILEC. JAAZ. JA8SS. KH6.
 KLTGAF. OH7NP. VESBN. LE1UU. YU8BC.
 YV1AD. I045P. ZB1CU. ZMMER. Dave Jenkins
 follows with HB8NL. KP4BA. GJ4F. F77J.
 G8UT. PA0KB. KZ5YS. DL9TJ. G6ZO. F6QJ.
 and GMDMG.

14 Mc Cx Alan 5CX PXIEKX XWBA8
HRAAS* HRAIWH* HK4BD* KP4* VP8*
CMRAA* ZBIBF* VQ4EO* HB1KU/HE*
Z86* Z55* XEIMB* SUIDD* XEIOE* V56*
CNRA8* and ZAB8B, AC3PN, ZDZNVW/ Neil
38G VQ9CB* Allan 3WL G8* Jack 3A:
G8* DL* G8* II* DUDDO* VUIMA*
G8* H8B* G8* H8ZFL* HRIAT*
Z86C* KTIEXO* V88* LA* UZ83*
F8B* CR8* Z33* GW* TF8TP* AP49* HB4
Ken 3KR: HB1OP/H8E, OZ* G8* F8* EA

Listed below are the highest twelve members in each section. New members and those whose totals have been mended will also be shown.

Call	Cer. Cnt.	Call	Cer. Cnt.
No. rises		No. rises	
VK18Z	3 175	VK3ATN	26 153
VK4HR	12 178	VK4KS	9 152
VK1RU	2 168	VK6KW	4 150
VK4PJ	21 164	VK1LN	11 141
VK3KE	10 162	VK4RW	23 141
VK3JD	1 155	VK3AWW	14 140

Call	Cer. Cnt. No. rises	Call	Cer. Cnt. No. rises
VK3RZ	6 222	VK3CX	86 175
VK3PH	35 205	VK3HY	45 172
VK4HR	8 200	VK3EO	2 170
VK3CB	10 200	VK3RX	23 160
VK4PJ	29 191	VK3RU	18 158
VK4PL	9 178	VK3RO	29 157

VR330	40	142
		Amendments
VR331	30	143

ORAN			
Call	Cer. Cnt- No. ries	Call	Cer. Cnt- No. ries
VK3BZ	4 331	VK3NS	16 195
VK3ACX	6 225	VK3HG	3 181
VK4HR	7 214	VK4EL	10 178
VK4FJ	32 206	VK5KW	13 171
VK6RU	8 203	VK3DI	2 170
VK3JY	13 199	VK3JY	

VR3XD - 61 260 VRACC - 63 117

DE, PIZAN LA V1R2 V56; II, XEIMJZ
DI/DL YU, KG4AV, SM, OH, PWTYO
45W7P Z86 QZOWD, W4QAB, M1PDL
45W7P Z86 QZOWD, W4QAB, M1PDL
KVA4A Europeans Albion PCG
58AX4, Gs, I, OE, DI/DL, OH, YU
V1R2V, XJDI, E13L, VPHB, FBRH
PIZAV, EA John ZC8 XE, DL JA, ALB
IAHM ZC5CT, PIZAV, 65AX4, XH2FL
V1R2V, XJDI, E13L, VPHB, FBRH
G, OH, DL, PA, HB, F, OE, EA, OZ
YU, SM, V56, KR8, KA, Rob 45W7P
HAB, K247F, P, OH, YU, DL, TIDPZ
VQOFO PIZAV, EA HBH, YU, DL
4X41F PIZAV, CT1 C38R John AH1
TILBC TIBZ, KPAACB, FOSAL, IS17C
V1R2V, XJDI, E13L, VPHB, FBRH
SL, I, OH, G, PA, OE, HBH, KVA4A
FBBXK CTJCI, Z86D, JA, Jack H69
DI/DL YU, KG4AV, SM, OH, PWTYO
II, JA, XJDI, KILTP, G, GW, H69
OH, OH, PAO, SM, V56G, YSDRG
V1R2V, VPHB, VPHB, VUSC, VUSDF
V1R2V, XJDI, E13L, VPHB, FBRH
HBH, F, CM, VY5BZ Z86C, XW8A
COBCT Z81B7 FK8 KH8 KVA4A
V1R2V, VPHB, VPHB, VUSC, VUSDF
FABGA FK8 K8C KUL KUL
KRGW KWBW KVB4L JA, L1ZMCA
OE, OH, VPIBR SM, V56G, VSDRG
V1R2V, XJDI, E13L, VPHB, FBRH
58AX4 Inn WIA-13007 LUSKA LUSKA DL
Jankin VPHBZ KJ8 DL YU2MA, KVA4A
V1R2V, XJDI, E13L, VPHB, FBRH
CTJDI VY5BZ, OH, II, KVBH, JA, KPTF
CTJDI VY5BZ, OH, II, KVBH, JA, KPTF
CTJDI DUAIG 3AHN OE, G, YU, SM
XEIMJ, HBSC, THRE, DLIDJ, 65AX4, X

14 Mc. Phone SHQ: Gs, ZBIDHF/VS;
ZC8CT, GW, SATZ, PA, HKADP, CE2DD
CTI, SBL: Gs, IJA: ONA, PKAR/MM,
G, GW, SM, HBIOF/HE, CENMM, I;
XZ3SS, HKADP, 45TYL, VUZCR, TG2AD
HCIES, PYCKP, PYZANS, PYINC, PY4VX
PV4ZS, XZ3CP, HKADP, LUDDM,
LUAAAT, EK2CO, DJL, PIJJ, F, EA
LUFAAE, CX6PV, KJJO, NKE OE, HK3CP
G, SPG VNM, PKADP, Snn NE, CE2DD
COABL, DJL DL, F, HVA, FMTWS, G
HBIKU/UTZ, Hpts, RYV, HVA, FMTWS, G

KXK4P H2 K1KPF K1KPF KV1KZ KZCZC 31H1H
 OZ OM 02 P111 SM T1JRMZ VP0G
 K1KZ V1U2R KZANT SAITA SASZC
 Harold
 COIAF F VQEOZ SAFTX 11 ONZ E
 OZ OM H1KZ CNP11 CNMNA KL1S KAJTA
 K1KZ
 KXK4P GW PAO KZCNA CRBAH ON
 H1KZ 6ST KZKZKN P1JCH 384X
 G1W1K
 H1KZ 11KZ 11KZ 11KZ 11KZ 11KZ
 N11 QGSH1 ETIUS KR6 OZ 11 U
 ONZ OZ OM HKSFV TGBAD KZCZC
 SASZC 8WO SASZC SAITL 11 F HKADF
 KV4BB HKSER J1T1H CLX OZ SM
 K1KZ
 HKMPC TGBAD T1GCHV LUDMG
 KZCZC P1Y1H1S LUTAA PAO H1KZ
 K1KZ
 AC3CQ OH KA 157 David KZAT
 K1KZ 6 11 GW CTI OH HERS11
 K1KZ
 OZ C2C5C 71S1G VSE AS1 W1A11
 K1KZ
 H1KZ 11D1S1T VY1S1R ZM1AT LUTAA
 G1D3FAC GW Red 11 KZCZC EADT
 L1D K1KZC HC1OM HKKZC KV1B1
 OMAAQ KX1AX V1R1C
 K1KZ KA KR1E KA KV4BB

H Mo. 3JA, Wa*, KH5*, KG6*, V88* 3PG
 JAIANG*, DL8AL*, Wa*, WORFT MM*
 HCIEP*, HCIF5*, YV5AR*, ZPT5B* Frank
 SEU, Wa HC, V80, KR6, KN9, KA, VR2
 SANC, W*, CP5EF*, KR6*, HCIEP*, KV4BB*
 Len JALD W*, and G. DL, KA, JA, V88
 CR5AH, KR6, 5WO: G5VT, WIEWS MM*

CO1* TL2: HC1F8*, VP8BD*
 27 and 28 Mo. 3PG reports Ws around 8000
 to 0100s and VK9BW*. SEU heard W6VAD
 W5VY. 4XJ spent some time on these bands
 with these excellent results: T13LA*, KH8BQ*,
 W8AA*,

XHBAGY*, XHBAVH*, XHBBIM*, XHBBAK*
W4NHFF*, K4BZJ*, W4PQW*, W4BWP*
W4WSJ*, K4BLM*, W4NJM*, W4WWJ*
W4EKZ*, W4HZG*, W4WAQ*, W4UCY, W4AZO*
W4SVY*, W4ITC*, W4UMLW*, W4TGM*, W4KJC*
W4W4W*, W4W4W4*, W4W4W4*

Rare QSLs were received by RAMB VKIDY
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX
8CX FBEXC YNIAA, VKIDY SHG FYBX

Thanks to WFFY, the Northern California
DX Club and Vks 2AMA, 3CX, 3HG, 3HL,
3LA, 3KKR, 3MH, 3PG, 3TE, 3WQ, 3XB, 3YS
3ZC, 3ZO, 3ZU, 3APF, 3ALC, 3AHM, 3ALD
3RW, 3CF, 3IL, 3RK, 3VO, 3EL, 3LZ, 3JAT
3KCU, 3RRS, 3L-3MM, 3VLE Jenks
3KCU, 3RRS, 3L-3MM, 3VLE Jenks

were they in fact that not one member dropped off for even a tiny little snore, but they kept firing Mr Burton with a barrage of questions which he was most willing to answer. The lecture with which he demonstrated his equipment with which he demonstrated his lecture included two C.R.s. which were the envy of all present. At the conclusion of the lecture, Fred JVS thanked Mr. Burton for his excellent lecture and members showed their appreciation by a very solid round of applause. During general business, the President announced that a new Secretary had been appointed to take over Col SPO's position, as Col, after his marriage, will be moving to the country to try his luck. Cheerio Col, and good luck in your new venture and lots of good wishes are extended to you and Phyllis for a very happily married life together. The new Secretary will be Len Robinson, SAID, and we hope you'll enjoy your position Len; it will be a lot of hard work, but we're sure you're the man to do it.

The President welcomed three visitors to the meeting, they were Doug Twigg, VL, ex-III, who is to be the radio supervisor at Macquarie Island in the new team going down to the south and who expects to operate while he is there and will be taking out a call for the trip, also Barry 2ZAG, and Mr. C. W. Searby, who hopes to become an associate member of the Institute shortly. New members to the Institute were welcomed, these included Neil Town (3ANK) as a full member, and the following associates: Morris, D. Weston, A. Wright, R. Strachan, R. Kidgell, M. McDonald, N. McDougall, E. Bailey and T. Phadry.

Certificates to those successful in the National Field Day were presented to John 3ARJ, Hans 3ARH, Alf 3IK and Fred JVS, also to Eric 3EL for his success in the Ross A. Hull Memorial Contest.

The lectures for the next general meeting to be held on 2nd November will be by Mr. George Glover, 3AG, whose subject will be "Communication and Ancillary Equipment for Home and Portable Use." Together with a practical demonstration of the equipment. December meeting (7th) will be a family night with lots of fun for men and the kids. Don't forget the Annual Dinner to be held at the Hardware Club on Friday, 4th November. Tickets are obtainable from Max Hull, 3ZS.

Over the last couple of years a small group have been adding variety to the Annual Convention by making it a camping week-end. It

is such a saving on hotel expenses when you have a family and can be such a lot of fun with a crowd. Mum and the kids go to the pictures while the Olds have their meeting, then they all join in with the activities on the Sunday. We expect to have about five or six families this year with either caravans, tents or converted trucks. The meals are easy, all you need to bring is breakfast for Sunday morning, the dinner on Saturday night and midday meal on Sunday can be had at the hotel, but don't forget to let Neville 3ACN know what meals you'll be needing and for how many, and also how many seats you need booked at the pictures.

Fred JVS managed to get brother Jim 3ABA safely married off earlier in the month and Jim and new VYL Vera have been happily honeymooning in the vicinity of VK's "Our Arbour" and "Our Bridge." Well that's another good man gone west, however we're working hard on Vera trying to give her the right idea in regard to this Amateur Radio. Can't seem to get that 3VZ off, he seems to believe

in safety in numbers, it's not that he can't hear to be tied down to one girl, he just can't drag himself away from all the others. Max 3BQ is a grandster again; son John, who has been attending the A.O.C.P. class this year, has a brand new daughter.

The Bi-monthly Victorian Scramble held on the first Monday in October got away to a good start and was very successful on all bands. Those who were operating in the Scramble found it a most enjoyable change to the normal contests and were very enthusiastic about the whole idea. However, we would appreciate more activity, particularly from the country stations. Between now and the next one, which will be held on 5th December, pass the word around and get it known. Remember the more stations operating, the more interesting it will be for all. The rules for the Scramble appear in the September issue of "Amateur Radio." The results of the October Scramble will be announced later—Phyl Moncur.

80 METRE TRANSMITTER HUNT

A lovely sunny afternoon brought out a good attendance to the 80 m. Tx Hunt. At the starting point the compellers were a little confused as there appeared to be two signals, one sending "de 3WI" and another, in the place of the long dash on the normal cone wheel, was sending "de 3ADU." The 3ADU tx was very much louder than 3WI, but fortunately both appeared to be coming from the same direction so all competitors moved off towards the north-west. On getting in the vicinity of the location, however, they found that the two tx's were situated some miles and a half apart and Eric, listening to the 3WI tx, was hand sending 3ADU from a Type A tx during the time 3WI was off the air. The actual 3WI tx had been concealed in a paddock of thistle bushes at Kellor and a co-ax line led to the top wire of the nearest fence. The winner was ELN who took an hour and a half to find it, followed nearly an hour later by 3ZAD second and 3QJ third. It was certainly a hard one, but very interesting all the way.

The group, which numbered 36, then squatted down on the grass in a big circle and had afternoon tea together and a chat. These hunts are certainly an excellent way of getting to know the other Amateurs and their families. How about coming along to the next one which is to be held on Sunday, November 18, commencing at 2.30 p.m. from the plantation

Please Note the New Address of the INWARDS AND OUTWARDS VK3 QSL BUREAU

C/o W.I.A. VICTORIA DIVISION,
191 QUEEN ST., MELBOURNE

QSL Cards for VK3 are being handled from the Victorian Division's rooms at the above address.

QSL Bureau Managers and members are requested to forward all future cards and correspondence to VK3 QSL Bureau, C/o W.I.A. Victorian Division, 191 Queen Street, Melbourne.

YOU HAVEN'T
BEEN HIDING
OUR LIGHT UNDER
A BUSH!!

You may think that the TRIMAX Range of components is decidedly limited, but nothing is further from the truth! We do not seek to present a full range in our advertising, but rather prefer to offer you a most comprehensive catalogue of selected components, from Audio and Power Transformers to Electrical Connectors. The December, 1954, issue of the TRIMAX CATALOGUE saves you leafing through old magazines! So . . . SEND FOR IT TODAY!

TRIMAX TRANSFORMERS

PTY.
LTD.

Corner CHARLES ST. & WILLIAMS RD., NORTH COBURG, VIC. — FL 1203

N.S.W.: University Graham
Instruments Pty. Ltd.

SYD. AUST.: C. N. Muller
Pty. Ltd.

QLD.: C. A. Pearce & Co.
Pty. Ltd.

WEST AUST.: R. D. Benjamin

A MUST FOR EVERY RADIO ENTHUSIAST

WORLD RADIO HANDBOOK

FOR LISTENERS

BY JOHANSEN

Price 15/9 and 9d. Postage

This book contains a wealth of information and includes Long, Medium and Short Wave Stations of the World, Frequency Stations, Broadcasting Receivers, etc.

OBTAIN YOUR COPY NOW FROM—


McGILL'S Authorised Newsagency

Est. 1860

183-185 ELIZABETH STREET, MELBOURNE, C.I, VICTORIA.

"The Post Office is opposite"

Phone: MY 1475-7

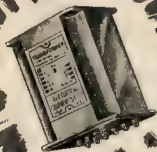

A & R OUTPUT TRANSFORMERS

★ TYPE 921 (921-8: 2 or 3 ohms; 921-15: 3.7 or 15 ohms):

For VALVES:

507, KT66,
etc.

Suitable Conversion

"WILLIAMSON" to U.L.

See "Audio Engineering" of
June, 1955.

30 WATTS. 20-30,000 c.p.s.

Primary: 5,500 ohms.

SCREEN TAPS: 10% of Plate Z.

F.R.: Plus or minus 1 ohm 10-50,000
c.p.s.

Leakage Inductance:
15P/15P: 15 mH. maximum.
Prim/Sec: 20 mH. maximum.

★ TYPE 931 (931-8: 2 or 3 ohms; 931-15: 3.7 or 15 ohms):

For VALVES:

6L5, EL87,
KT66, etc.

See "Radio and Hobbies" of
February, 1955, 17 watts
U.L. Amplifier.

30 WATTS. 20-30,000 c.p.s.

Primary: 4,500 ohms.

SCREEN TAPS: 10% of Plate Z.

F.R.: Plus or minus 1 ohm 10-50,000
c.p.s.

Leakage Inductance:
15P/15P: 15 mH. Maximum.
Prim/Sec: 15 mH. maximum.

★ Ultra Linear Output Type—

Type 918—12 watts.

Prim.: 5,500 ohms p.p. (with
screen taps).

Sec.: 918-8: 2 or 3 ohms;

918-15: 3.7 or 15 ohms.

Type 940—12 watts.

Prim.: 8,000 ohms p.p.

Sec.: 2, 8, 15.5 15 ohms.

Response: 10-50,000 c.p.s.

Valves: 6V6, 6BW6, KT6L,

EL84, etc.

10% Screen Taps.

PERFORMANCE

DEPENDABILITY

APPEARANCE

QUALITY

**FULL DETAILS FROM
THESE EXCLUSIVE
A & R DISTRIBUTORS**

MANUFACTURED BY—

A & R ELECTRONIC EQUIPMENT CO. PTY. LTD.

378 ST KILDA ROAD, MELBOURNE, VIC.

Details from these EXCLUSIVE A & R DISTRIBUTORS!

QUEENSLAND:

A. E. Harvold,
123 Charlotte St., Bris.

TASMANIA:

Homcrafts Pty. Ltd.,
220 Elizabeth St., Hobart

WEST. AUST.:

A. J. Wyle Pty. Ltd.,
1011 Hay St., Perth.

SYDNEY — N.S.W.:

United Radio Distribu-
tors P/L, 170 Phillip St.

Homcrafts Pty. Ltd.,

100 Clarence Street.

SOUTH AUST.:

Garard & Good-
man Ltd.,

196 Rundle St.,

Adelaide.

MELBOURNE & VIC.:

J. H. Macraith & Co.

Pty. Ltd.

Homcrafts Pty. Ltd.

Motor Spares Ltd.

Radio Parts Pty. Ltd.

Warburton Frank Ltd.

In College Crescent at the rear of the University? The December Hunt will be held on 11th of that month. If you are not equipped with 20 mX receiving gear, come along just the same. It's a lot of fun, and it's sure to get you enthusiastic about building some gear. We can guarantee the family will enjoy you there, as they are always in the children. The Tx Hunts have been known to completely convert anti-radio XYLs. During the summer months, with the warmer weather and the long days, it's a lot of fun to be along a picnic table. Hope to see you at the next hunt.

SOUTH WESTERN ZONE

Once again there is not much to report, in fact not as much as last month. I don't know what has gone wrong with this zone, never hear our Secretary on the hook-ups or for that matter, 3BXH. He may be busy, or I'm about showing a little more interest in the zone affairs otherwise we will be a dying race. Heard quite a lot of the boys in the Contest. Bill Wilson has been very active on the 20 mX band, having logged DLUX, DLATU, WTAAT, WEVZ, PYAVX, VEs and many others. Suddenly, I have heard no one from the zone presented, in fact haven't heard anyone on it from this zone for a few weeks. I listen to Don ALQ on Tuesday nights; glad you had a good time at the Albany Hunt. Don ALQ is fairly regularly. John 3ANJ is building a three stage rig so it looks as though the ATS will be coming back. Les 3ALE is not very active as he sees enough of radio all day; his XYL is sick of the ATS in the lounge, so best not get in the little r.f. into his ears. 3EQ hasn't been very active of late owing to pressure of work in the picture industry, but hopes to be able to devote a little more time to radio shortly.

Haven't heard Gordon 3AGV on lately; how is the Convention arrangements going? I hope you have a most successful one. I saw 3AHJ was in Ballarat recently and saw Bill 3AMH; he informed me that he was shifting to Bendigo as it was promotion for him with the E.C.C. of Victoria. I hope he will be in November. He will most likely be at 3AQN's QTH a lot.

NORTH EASTERN ZONE

Doug, well known formerly as 3JL of Malgore, has transferred his position at Cambridge, Tas., to the Dept. of External Territories and is going to be in the party to do the 1950-51 tour of Antarctica. I hope 3JL will be leading a quiet life; Keith 3JC is busy on his house. Stan 3AGT is in comparative isolation at Tugue, where Les 3ALE is able to keep in touch with other zone members and hear how Bruce 3AGG gets on with the DX after modifying his rig. Ted 3AOB is concentrating on the 30 mX band. Colin 3AC is active to local v.h.f. skeds, while Alex 3AT is playing with colour photography, and Secord 3AC is working on his motor cycle.

Jan, our local former PAD, has a good tx in action, as a step in the right direction. We regret losing John 3ZBG, from Numurkah. Vern 3AXW has his troubles with h.c.l., while Col 3AW has overcome a similar type of trouble with traps, etc. There are two Associate membership "prospects" in Cobram at the moment. Vic 3ZC is ready to rejoin the zone, while Frank 3ZU will be away on leave, carving, shortly, and Jack 3ACB should have just finished his. Des 3BP has been heard working on the 20 mX.

Bill 3AWQ has obtained some Command equipment from Jim 3KJ, prior to getting on the 30 mX band. He has a 30 mX 20 mX DX. Jack 3PF has handicapped out by phone by difficult circumstances "pro tem". Vic 3ABX has been the distance. It is hoped that George 3GD is getting a go at the 15 and 20 mX DX, that is where Hugh 3AHF fills in his time. Bill 3ZL is all for this DX business now. It is hoped that Keith 3AKR will be able to complete his A.O.C.P. by passing the Morse.

EASTERN ZONE

Most important news is the formation of the Latrobe Valley Radio and T.V. Society. Members of the Zone, Gippsland Radio Society went to the meeting. There were 18 in all, where 29 enthusiasts were present. The Zone President, Bert Budge, took the chair and it was decided to form the aforementioned society. Jack 3ZC was elected President, and Jim Quig, Secretary, Ian Dunelcliffe Vice-President. A simple objective was resolved: "To further the interests of the W.I.A. in the Latrobe Valley".

Meetings will be at 8 p.m. on the second Friday starting with Nov in October and as decided. Membership is open to anyone who is interested.

The E.G.R.S. will have a technical film night at home, Anderson's home in Stratford on third Friday.

Jim Quig, of Morwell, has passed the Limited exam, and he has built an ft. 1. v. rx which is anxiously awaiting a signal. Ted 3ALA has a junior op., son, now and Alf Mackrell has another. 3SB has had a working be on two Sundays previous, when 3AHK, 3JO, 3AJA and Doug Anderson came over and helped push up the signal, which some day will support a 144 Mc. beam.

Our zone hook-ups on 3650 Kc. at 2000 hours on Sunday are still popular, but we do miss our old friends. What about a brief appearance, boys?

CENTRAL WESTERN ZONE

Our Convention was held in Nhill on Sunday, 10th Sept. We were lucky in picking a nice sunny day and all functions were arranged by Herb 3NR and we owe him a lot of thanks for the way everything worked out.

First in line of the their gear and had contacts with Clive 3ACE in Birchop. After an excellent lunch, we paid a visit to the Aerodrome and were shown over their equipment which included M.L.E., etc. We must thank the staff for going to so much trouble for us.

At the annual meeting the following officers were elected for the coming year: President, James Farrer, 3DP; Vice-President, Herb Brown, 3NN; Sec. and Treas., W. J. Kinella, 3AKW. There was very much business brought forward so the meeting soon finished and we again journeyed out to the 2 mX location and enjoyed the sun.

Trev's (3ATN) and Ray's (3ATN) gear looked and worked extra well. Herb also had mobile gear and his junior op., Gerry, is very keen on the Amateur radio. Trev, which he has already built it a credit to him.

We had another meal and then were shown over the North Power House by Alf 3CH. Some of us had to leave early, but most members were able to stay until the end, after a very enjoyable day.

Those present were VKs 3ATR, 3AKW, 3IB, 3NN, 3ARM, 3ATS, 3CH, 3EF, 3APO, 3AKP, 3ATN, Jeff Oster, Lyne Schultz, Jack Pulman, Gerry Brown, and David Goldsworthy.

PHONE NUMBER CHANGED

The telephone number of the W.I.A. Victorian Division has been changed to: **MY 1087**

GEELONG AMATEUR RADIO CLUB

The 2 mX enthusiasts of Geelong were given the secrets of crystal control converters by Ed 3AKY, who presented a really interesting paper. Ed's success on 2 mX over many years, and the clear elucidation of many aspects of v.h.f. activity generally, will meet future impetus on this band by local members.

During Hobby Week in the metropolis, the boys took the opportunity of visiting the W.I.A. stand and enjoying a rag-bash with the city boys. A further highlight of the club's activities was a second talk by John 35Y on t.v. It was a really good one, and the boys, with modern techniques in this field and is passing on his experience among the boys.

Jim 3ZBR is experimenting with a new converter and tx from his QTH near the Yu Yu Melbourne stations please note. Fred 3ALG has a new secondary standard—a 100 Kc. one—made in 1930. Chas. 3XK is batching and manages to pound the ether. The other stalwarts 3BU, 3WT, 3AET, 3ALP are on at regular intervals.

QUEENSLAND TOWNSVILLE AREA

Sorry boys that the notes did not appear in October—on eight weeks' leave. Opportunity was taken to attend the Exhibition in Brisbane during August and a few of the local boys were met during the visit. Unfortunately the monthly meeting was being held two days after I left so could not meet many others. Quite refreshing to see notes appearing from other parts of Queensland; keep them coming in, as we all know what is happening in each district.

Two meetings have been held of the T.A.R.C. since the last notes. Attendance not quite as good as expected. Glad to report that I have last a student course for the A.O.C.P. has started with seven members and hope they will last.

Next meeting will be held on 17th November when the lecture will be on Frequency Measuring in local areas. The next meeting on 15th will be visit to the Regional Electricity; 4RU will be conductor.

During the latter part of August the air was disturbed by a strong signal on 7072 Kc. from 4DK located at Ayer. Welcome to the bands John and may your signal never grow weaker; 4DK is a lot of fun. There are large crowds round table on 7 Mc. each Sunday, the boys from Atherton, Mareeba, Cairns, Townsville, Cairns, Brisbane, Melbourne, and Rockhampton being to the forefront.

4EL and 4BE chasing the openings on 21 Mc. while 4LR, 4JR, 4RW and 4WH are on 7 and 4BE is on 21 Mc. with his new shortwave beam. 4EL and 4BE looked in good form. 4WE; you forgot me Lance. Our old friend and ex-Secretary of the T.A.R.C., Ken Nutt (ex-4XD) passed through our district on his way to Mania to Cairns to take charge of the local "B" class station; welcome back Ken—4RW.

MARYBOROUGH

4CB and 4AI thinking of getting back on 6 mX. 4BG is already there, looking for the first break-through. 4CB bought length of co-ax for his future 20 mX beam. I am not to mention that it was expensive in case his XYL reads these notes. What a pull! 4BG waiting for co-ax to arrive. 4CB remains on the traditional fox. 4EX beam. 4GH improving the layout of his shack and can now walk into it. Contemplates further improvements that will permit him to turn around. 4CB is on his way to Sydney for a u.h.f. course; lucky lad!—4BG.

SOUTH AUSTRALIA

Well, long suffering Amateurs, the hot potato seems to be back in the President's lap, so he has decided to remain in the traditional fox. He has to have dinner, Les, let's enjoy it together! Jack 3JD, Federal Councillor and crisis-prone, has decided to take a trial fly on tanker to Singapore. Once a sailor always a sailor they say, Jack. Anyway we hope that it is worthwhile, and that you will return to us ready to spar with our traditional foe, the SPB. Frankly, I reckon that you weren't game to face me after I had put Pincoet wise to you when I conjoined with him in Melbourne.

And whilst on that subject, my thanks to Federal Executive for the time and good hearing that they gave to me. I am sure that Dennis, the VKS President, and all the members of the Magazine Committee for their wonderful hospitality. The visit to the Model Exhibition came as a climax and would like to congratulate those who were responsible for such an excellent set-up. This opinion may be biased, but I think it was one of the best and even my XYL was visibly impressed! After that little homily, when are you going to invite me to the Golden? I'd dearly love to spike Warwick's guns.

By the way, the residence of SPB has had its lifted during the Saturday afternoon's meteorological disturbance. We saw him there afterwards and he remarked that he must be getting old because he didn't have enough heart to get up the stairs to his room. I'm sure he's house! Our sympathies to Mrs. SPB—don't let it spoil those banana cakes, Audrey.

The general meeting last month was well attended to welcome back the President, now a dual citizen of Victoria and New South Wales. Some of the boys' films were shown. Taken on spec, they turned out to be quite an interesting evening's entertainment. Our thanks to those who supplied and Dougall 3BY and Norm did the honours.

The R.D. Contest was well fielded and our top six runners really made the pace hot this year. Very fine effort chaps, and this Division's grateful thanks to those who sent in their logs—some 87 of them—to back up the finest effort that VKS has ever made.

The time of the comp., the Walrus said, "to speak of many things," and that reminds me that Council will soon be looking around for some lecturers for 1950-51. Anyone that can supply technical lectures or who has completed ideas please pass them on to yours truly. Don't wait until June, 1950, because the programme has been prepared. It is about time somebody came forth with a transistor 144 Mc. tx and rx. What about you Ian?

The Classes seem to be proceeding according to plan and we are very grateful to those who have taken the course. I am sure that the course instructors, Carl, who is out of hospital and looking well again is keeping a fatherly eye on the boys. The next step is when a defaulter (me again) fails to attend the class. By the time you reach 14 w.p.m. chaps, you will have copied 17) the lists of SMD, 5JD, 5OR, 5AR, 5SR, 5BR, 5DR, but not least, 5KU (no comment from SCA, please).

The Sunday morning broadcasts were taken by John SKX, our Vice-President and I. I am sure that these broadcasts gave me a great deal of pleasure, especially the contacts afterwards with the chaps, however short they may be. So do be backward in popping up onto the band. SWI is usually on ten minutes or so before-hand.

George SBC, at Lulu's, is doing a fine job in the Bush Church Medical Aid Service, looking after the communications side of the business. He hopes to be down to collect a new microphone in October so we may hear more of him; has even made A.B.C. News for his work on transceivers for the fishing fleets. Good going.

Called into Remark on the way home and had a yarn with Hobby SRL, who was up to his armpits in concrete at the time. Fred SMA was also there, and I was surprised to find when he appeared at the meeting. Roy SDA and Bob SSG both at the same meeting—presumably the lightning had scared him out of SFI. Hughie SBC was also on leave from SRM, but I had a yarn with Harry SKW and he let me into the secret behind the door Hughie. It all looks very nice to me, but of course is unmentionable (a 2 mx tx) in these notes.

Jim ZBO (ex-SUL) sends his regards to the VKs from Goulburn and looks a bit contented in his new digs. I am sure he will not get blown clean through us all, but Jim and his XYL thawed us out with a grand log fire and a brew of tea.

EVER'S PENINSULAR

Wally SDF, from Pt. Lincoln, reports that he is back on the air with the distant ATX. It certainly sounds f.b. Associate Alf Mack graced the meeting place and reports that he is studying hard for the A.O.C.F. Exams. Very little heard of Jack SVI these days; comes on for a rag-chew now and then and declares he's not coming away. Apparently Wally has better grape-vines than the Adelaide Plains for he reports that Darcy SHV in Kadina is about to have 30 cycle power. Perhaps Les SUX will shift and rejoin you all.

SOUTH EAST AREAS

The monthly meeting was postponed and so misses these notes. Activity, like the weather, seems to be at an all time low, although Les SAG and Ray SJA were on 2 mx. The meeting complete with mobile gear, was in the Mount on 15th Sept. and from Les' QTH established a two-way QSO with Rex S2AB. Les' signal, copied Les 5 and 7 with Ray's signal also audible and coming from a halo antenna in his car. Claude SCH has been heard on 40 mx with a new rig. The time of the day is 11:00. I missed you Claude, but since Mohammed came to the mount and missed out, it looks like the time of the day will be 11:00. Mohammed next time doesn't it? Have you ever used that one, Warwick? Col SCJ is on holidays. All the h.c. station engineers seem to be on holidays—how do they manage to keep going? Ah! I've got it, they're all going automatic!

Rex is still battling with storm damage, but we understand he should be soon on 20 mx complete with beam. 20 mx quite good and a few more miles. I am sure that Tom SFW has been settling into his new QTH, but still manages QSOs on Monday nights. Stuart SMS has spent a lot of time fiddling a VR1 to his v.h.f. rig and the time this printed will have left his mark on the VK-ZL Contest, no doubt. The beam still needs adjustment. A view from the QTH to the XYL during September brought forth a lively discussion on DX and antennae. These are the things that stick out from a better's eye, aren't they Stuart? Better antennae and receivers should bring their reward to the 2 mx gang also.

Worked Jack JJA from Hymn, with the result that Jack and XYL introduced us to Nullawarre's fine brand of scones and cream. Jack is a real find. I am sure that the amateurs that I had the privilege to meet and it left me feeling that this grand hobby of ours has something a lot further to offer than just the DX or the experimental aspect. The bond of real friendship that exists in Ham-down would solve all the international problems and would be extended into the realm of power politics.

And one final word—if the compilation officer blue ink has been on the pen, then I am sure his "A.R.s." and even might go so far as his p's and q's also!

It is that the VKs boys are getting odd, or they giving things away, or are they only interested in the untimeliness of wedding bells? According to our spy (unpaid) in VKS this time of the day is 11:00. Perhaps a log was given away on 18th October, and is backing

up for a second helping when he gives Joan away on 24th December. Not to be out done, Frank SMZ is taking the long walk with his daughter Barbara on 8th November. Are the respective grooms members of the I.A.A.? If not, SFS still please follow us—Editor.

TASMANIA

This month the label suits and various summaries should be addressed to the compiler for this month's notes. Tiny TJD, the usual scribe, is rather snowed under with circumstances this time and isn't able to compile the notes.

At the general meeting held in the club rooms on 8th October a roll up of 23 members attended. The meeting was held in the absence of the President, and Bill Talt carried out his usual secretarial duties. The chairman welcomed Bob Foster to the meeting; Bob is an exp-VR1 and is presently at Cambridge Aerodrome. Business for the evening was mainly taken up by Federal matters, the main item being that F.E. requires a survey to be made of the coverage over the State of the slow Morse transmissions on 80 mx. TKA is running the present affairs and would appreciate reports from any listeners. It was decided to hold the first hunt of the season on Sunday, 8th Nov. the time to be 14.00. Only for the present by TAJ. In reply to my complaint that my v.h.f. gear was getting very warm through on-air field days, I received scant sympathy and the offer of tin of grease for the generator—or was it for something else?

Tom TFM suggested that a field day be held on the 14th November to foster the building of equipment suitable for emergency working and after much discussion the matter was left for investigation in the hands of TAJ and Talt. The matter of commercial stations in the Amateur bands was raised and discussed and members were requested to log the stations that can be identified for handing over to F.E.

At the conclusion of the business section of the meeting a lecture was given by Joe TBJ entitled "Conversion of Converter to the Frequency Bands." As usual Joe had his subject at his finger tips and presented a theoretical method of conversion of 80 to 10 mx to 10 mx by using only three crystals. A vote of thanks proposed by Albot TAJ concluded what was to me a most informative and interesting lecture. But what it was worth.

Main event of this month is the arrival of the stork at the TDR residence with a double headed eagle. Let me state that the bird is The old wireless bird was also busy at Queens-town last month with a surprise for TJS—I forget what it was, now, but it was a big one. The TBR bus is again too, re-building the rig I mean. TAJM getting lower in frequency and now in the audio range at the best broadcast station in Australia for public use.

Many sore feet, aching backs and sweaty brows marked the conclusion of the recent rescue exercise held in conjunction with the Walking Club and Police. Doug TAJ had quite an experience when a light plane assisting the exercise crashed within a 100 yards of him. I understand that Doug was in the plane when he got out by the time he reached the wreck, or was it the result of the loss of the end of a finger on the terminal of the h.t. transformer? Any doubt about Doug's ability to handle time, but third time lucky. Insurance paid up Doug?

Associate Geoff Foster thinking hard about sitting for the ticket; come on, take the plunge and get your "A" done. Geoff has now finished the mobile 3 mx rig with a halo on the back bumper bar—simply brilliant. Geoff is now looking for a good idea to poke at the innards of a generator with a screw driver while it's going. TWS interested in H-S in building a vented transformer. TDR and TMR in with a.s.b. with something liable to pop up at any moment. Barney Watson learnt the hard way that you must learn to tune a transformer and not the feedback winding if best results are required. I believe about four hours of frustration took place before the house fell!

NORTH WESTERN ZONE

News from this area did not appear in last month's edition. This was because the writer had got a few letters a bit muddled and when he got them straightened out it was realised that there was insufficient time for the notes to reach Melbourne and the printer.

R.D. Contest has been and gone once more and this area was quite active. Ken TAJ made over 200 contacts and managed to get a few cws in between times. Others putting up a pretty good score were Roy TRN and Sam TWS. Did SDF and Ellis TWA were very busy this time of the day. I am sure that they had other business to claim their attention.

Ellis TWA has been busy this last month or so building himself a new 15—a real push job; although not yet completed, Ellis has been heard working Europe using only his driver station. He is building the new 15 and is going ahead with the erection of his 3 el. beam for 30 mx and hopes to have it working in a few weeks' time—TUV.

CORRESPONDENCE

The opinions expressed in these letters are the individual opinions of the writers and do not necessarily coincide with those of the publishers.

LIMITED LICENSE

Editor "A.R." Dear Sir,
For several reasons I did not receive my copy of Sept. "A.R." until recently, otherwise I would have written this to bring about the quiet to VK3BG. To put some of BG's statements back on the rails before burying the subject, may I say there is no "literary battle." Six letters in three months is not even a skirmish! There is no "dirty washing." Surely in agreeing with the remarks of VK3XU and VK3ZAO, only in so far as they concerned the L.L.s. and in stating VK6 is not diatoyal and why, is not dirty washing.

There is no "subtle reference" that my colleagues and I were "doing something for the electronic art" on the v.h.f. I stated I had never heard of TAJ H. This is not "inference" about the "epitome of Amateur Radio." Everyone knows that for many years the Ham has taken his lead from the laboratory of the v.h.f. He has used his own v.h.f. knowledge, and experiments with Ham gear, is, as I said, "breaking new Ham ground on the wh. with equipment the average Ham can afford."

Had VK3BG taken my remarks on their face value, he would have saved himself a lot of stressful words. And there is no need to worry about the "cancerous growth," because we have found the East has not got a monopoly of wire.

The L.L. subject has been discussed, etc., here and put into cold storage. Let's leave it there. Anyway, to VK3BG.

—J. C. Hoar, VK6OR.

[Correspondence on this matter is now closed.—Editor.]

HAMADS

1/- per line, minimum 3/-.

Advertisements under this heading will only be accepted from Institute Members who desire to dispose of equipment which is their own sole property. Copy must be received by 8th of the month, and remittance must accompany advertisement. Payment is made on the basis of an average of six words a line. Dealers' advertisements not accepted in this column.

FOR SALE: AR7 Receiver, complete with power supply, five coils, £35. Alternator 230v. 500w. Transceiver 1196A, converted, needs xtal only. Best offer. Wanted: three Link type 8 foot cabinets, also A.W.A. Class "C" Wavemeter, type R7647. B. Jellett, Hymn, S.A.

FOR SALE: Oscilloscope, R.A.A.F. type M/D52, complete with cables and separate power supply. All unmodified and as received from disposals. £15 packed for rail. J. E. Rogers, 61 Broadway, Yallourn, Vic.

FOR SALE: 5 new 826 tubes, £1 each. Wanted: Prop. Pitch Motor. B. Glassop, 343 Kissing Point Road, Dundas, Sydney.

SELL: Trimax TA906 100w. Modulation Transformer, as new, £6/10/-, Len Johnson, WF 2754 (Vic.).

WANTED: Coil Box C for AR7. D. Jackson, C/o D.C.A. Mess, Box 370, Darwin, N.T.

60 Watt xtal c.w. Table Top Rig. Custom built cabinet. Sell £25, or swap for Goodman's 150 or similar. C/o Harvey, MU 401 or LB 3883 (Vic.)

Homecrafts

PTY LTD

AMATEURS' BARGAIN CENTRE ★

TRANSFORMER BARGAINS

FERGUSON OUTPUT TRANSFORMERS

Type OP15 (32 watts)—

Primary: 6,600 p.p.
Secondary: 500, 250, 125.
49/6 inc. Tax

Type OP17 (32 watts)—

Primary: 10,000, 6,600, 5,000 p.p.
Secondary: 500, 250, 125.
49/6 inc. Tax

Type OP6 (15 watts)—

Primary: 5,000 p.p.
Secondary: 500, 250, 125.
39/6 inc. Tax

Type OP2 (15 watts)—

Primary: 5,000 p.p.
Secondary: 12.5, 8, 2.3.
39/6 inc. Tax

Type OP3 (15 watts)—

Primary: 6,600 p.p.
Secondary: 12.5, 8, 2.3.
39/6 inc. Tax

Type OP12 (25 watts)—

Primary: 10,000 p.p.
Secondary: 500, 250, 125.
45/- inc. Tax

CHASSIS BARGAINS

Black Crackle Punched Chassis

14½" x 8½" x 2½" and
13" x 9" x 3"

8/11 each including Tax

HOME CRAFTS for all High Quality Audio Equipment:

WILLIAMSON AND LEAK AMPLIFIERS WHARF DALE AND BAKER SPEAKERS THORENS MOTORS AND PLAYERS

Vented Enclosures — Speaker Divider Networks

Write for Quotations on anything connected with Hi Fidelity Sound

RECTIFIERS

Selenium Rectifiers, made in England

6 volts at 4 amps., 41/5 plus Tax
12 volts at 2 amps., 29/9 plus Tax

RECORD PLAYERS

comprising
Variable Speed Motor and
Crystal Pick-up in a two
tone leatherette case
100/- plus Tax

DIAL LAMPS

Boxes of 10 6-8 volt 0.3 amp.
5/- including Tax

SPAGHETTI

Yellow Varnished Cambric
1 mm.
3/- dozen yards plus Tax

WIRE

10/010 PUSH-BACK HOOK-UP
WIRE, 250 yard Reels.
87/6 plus Tax.

7/010 P.V.C. HOOK-UP WIRE,
200 yard Reels. 39/- plus
Tax.

TWIN FLAT FEEDER CABLE,
300 Ohms. 7/- doz. yards
plus Tax.

CO-AXIAL CABLE, 70 ohms.
1/6 yard plus Tax.

SINGLE SHIELDED 10/010
P.V.C. Insulation. 10/-
dozen yards plus Tax.

METERS

2 Inch Square 0-20 Volts
5 Ma. Movement.
10/- each plus Tax

SWITCHES

P.M.G. Assorted Types
2/6 each including Tax

290 LONSDALE STREET, MELBOURNE

FB 3711


from Italy..



..home of fine engineering of every type..

we proudly bring you

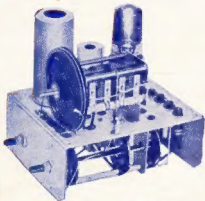RADIO COMPONENTS BY SOCIETA PER AZIONI GELOSO



Consistent with our policy of providing the Australian market with the highest quality and most economical range of components available, chosen from the world's sources, we now present some of the products of Italy's leading component manufacturers—**Societa Per Azioni Geloso**, of Milan.

The workmanship of Italian cars and many other products is recognised as being thorough and complete. The same technique has been applied to "Geloso" radio accessories and we proudly offer microphones, crystal inserts and V.F.O. units to discerning Amateurs and Experimenters, through normal Distributor channels, at very low prices.

Each component is fully guaranteed against defective workmanship and faulty material.

STUDY THESE OFFERS:

Transmitter V.F.O. Unit:

Type M4/101: A very stable five-band three-tube V.F.O. unit, fully wired and tested.
Bands: 2.5-4, 7-7.45, 14-14.4, 21-21.6, 28-29.8 Megacycles.
Dial: Fully calibrated and band spread over 180 degrees.
Tubes: 6J5 oscillator, 6AU6 isolator, 6V6 output (not supplied).
Output: Tuned on each band, giving at least 3.5 Ma. grid current to a single 807 on all bands.
Power Supplies (not supplied with unit); 400 volts at 32-54 Ma.
Price (including Sales Tax):

£10/4/9

Crystal Microphones:

Type M/100 Piezoelectric Microphone: A very attractive chrome plated "ball" type microphone of small physical size, complete with three yards of twin shielded low loss cable. Thoroughly shielded.

List Price: £5/19/11

Type T/100: Hand Microphone in well proportioned brown bakelite case. Unit fits on table without need for any stand. Uses UN10 fully screened insert. Complete with 4 ft. of twin screened low loss cable.

List Price: £3/12/-

Crystal Inserts

Type M400: Frequency response 40-7,000 cycles. Extremely robust and mechanically strong. Can withstand falls and knocks. No further casing is required as unit is complete as a microphone of attractive appearance.

List Price: 32/11

Type M410: Same unit as M400, but with extra screening to exclude R.F. pick up.

List Price: 38/6

Crystal Insert:

Type UN10: A complete crystal insert for incorporation in a cage in the manufacture of complete microphones. Used in microphones employed with Geloso wire recorders.

List Price: 30/7.

Full information from the Sole Australian Factory Representatives:

R. H. CUNNINGHAM PTY. LTD.

118 WATTLETREE ROAD, ARMADALE, S.E.3, VIC.
and 184 VICTORIA ROAD, DRUMMOYNE, N.S.W.